

# LM3402/LM3404 Fast Dimming and True Constant LED Current Evaluation Board

National Semiconductor  
 Application Note 1839  
 Matthew Reynolds  
 September 30, 2008



## Introduction

The LM3402/02HV and LM3404/04HV are buck regulator derived controlled current sources designed to drive a series string of high power, high brightness LEDs (HBLEDs) at forward currents of up to 0.5A (LM3402/02HV) or 1.0A (LM3404/04HV). This evaluation board demonstrates the enhanced thermal performance, fast dimming, and true constant LED current capabilities of the LM3402 and LM3404 devices.

## Circuit Performance with LM3404

This evaluation board (figure 1) uses the LM3404 to provide a constant forward current of 750 mA  $\pm$ 10% to a string of up to five series-connected HBLEDs with a forward voltage of approximately 3.4V each from an input of 18V to 36V.

## Thermal Performance

The PSOP-8 package is pin-for-pin compatible with the SO-8 package with the exception of the thermal pad, or exposed die attach pad (DAP). The DAP is electrically connected to system ground. When the DAP is properly soldered to an area of copper on the top layer, bottom layer, internal planes, or combinations of various layers, the  $\theta_{JA}$  of the LM3404/04HV can be significantly lower than that of the SO-8 package. The PSOP-8 evaluation board is two layers of 1oz copper each, and measures 1.25" x 1.95". The DAP is soldered to approximately 1/2 square inch of top and two square inches of bottom layer copper. Three thermal vias connect the DAP to the bottom layer of the PCB. A recommended DAP/via layout is shown in figure 2.


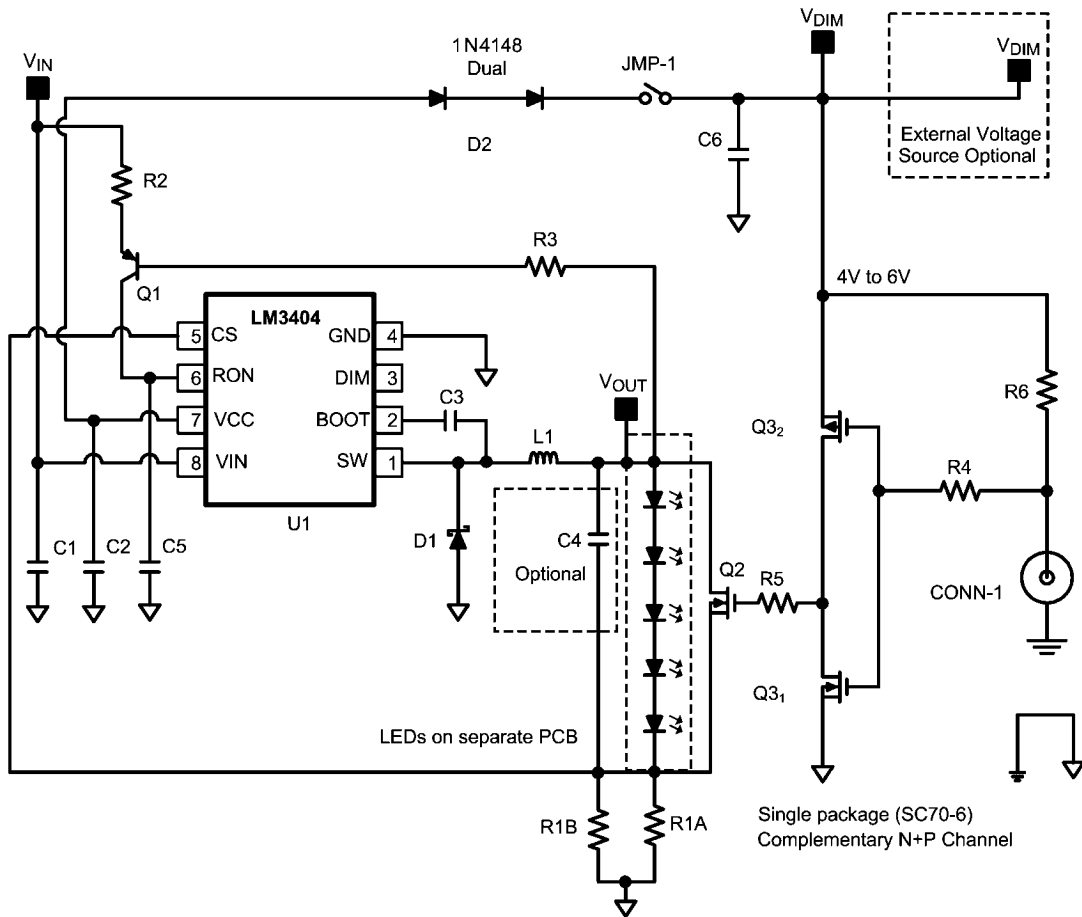


FIGURE 1. LM3402 / 04 Schematic

30061601

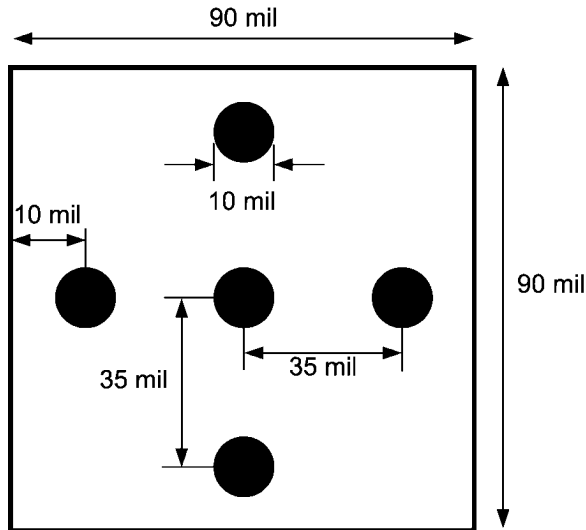

30061602

FIGURE 2. LM3402/04 PSOP Thermal PAD and Via Layout

## Connecting to LED Array

The LM3402 / 04 evaluation board includes two standard 94 mil turret connectors for the cathode and anode connections to a LED array.

## Low Power Shutdown

The LM3402/04 can be placed into a low power shutdown state ( $I_Q$  typically 90  $\mu$ A) by grounding the DIM terminal. During normal operation this terminal should be left open-circuit.


## Constant On Time Overview

The LM3402 and LM3404 are buck regulators with a wide input voltage range and a low voltage reference. The controlled on-time (COT) architecture is a combination of hysteretic mode control and a one-shot on-timer that varies inversely with input voltage. With the addition of a PNP transistor, the on-timer can be made to be inversely proportional to the input voltage minus the output voltage. This is one of the application improvements made to this demonstration board that will be discussed later (improved average LED current circuit).

The LM3402 / 04 were designed with a focus of controlling the current through the load, not the voltage across it. A constant current regulator is free of load current transients, and has no need for output capacitance to supply the load and maintain output voltage. Therefore, in this demonstration board in order to demonstrate the fast transient capabilities, I have chosen to omit the output capacitor. With any Buck regulator, duty cycle (D) can be calculated with the following equations.

$$D = \frac{t_{ON}}{t_{ON} + t_{OFF}} = \frac{t_{ON}}{T_S} = t_{ON} \times f_{SW}$$

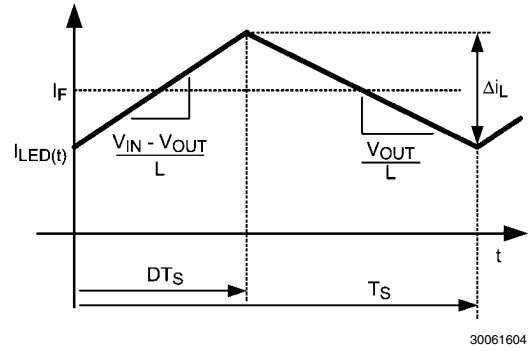
The average inductor current equals the average LED current whether an output capacitor is used or not.



30061604

FIGURE 3. Buck Converter Inductor Current Waveform

A voltage signal,  $V_{SNS}$ , is created as the LED current flows through the current setting resistor,  $R_{SNS}$ , to ground.  $V_{SNS}$  is fed back to the CS pin, where it is compared against a 200 mV reference ( $V_{REF}$ ). A comparator turns on the power MOSFET when  $V_{SNS}$  falls below  $V_{REF}$ . The power MOSFET conducts for a controlled on-time,  $t_{ON}$ , set by an external resistor,  $R_{ON}$ .

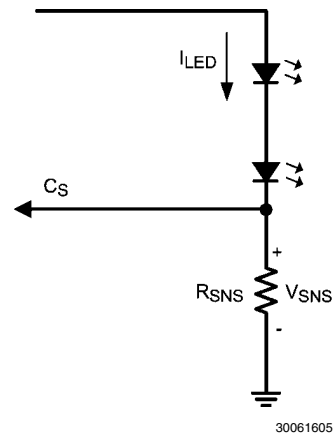

30061605

FIGURE 4.  $V_{SNS}$  Circuit

## SETTING THE AVERAGE LED CURRENT

Knowing the average LED current desired and the input and output voltages, the slopes of the currents within the inductor can be calculated. The first step is to calculate the minimum inductor current (LED current) point. This minimum level needs to be determined so that the average LED current can be determined.

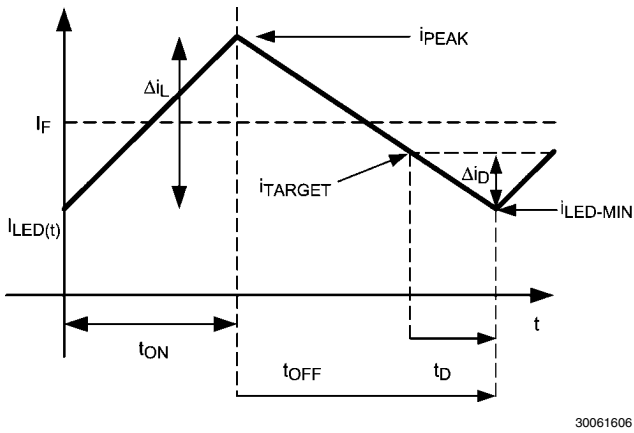


FIGURE 5.  $I_{\text{SENSE}}$  Current Waveform

Using figures 3 and 5 and the equations of a line, calculate  $I_{\text{LED-MIN}}$ .

$$I_{\text{LED-MIN}} = I_F - \frac{\Delta i_L}{2}$$

Where

$$I_F = I_{\text{LED-Average}}$$

The delta of the inductor current is given by:

$$\frac{\Delta i}{2} = \left( \frac{V_{\text{IN}} - V_{\text{OUT}}}{2L} \right) \times t_{\text{ON}}$$

There is a 220 ns delay ( $t_D$ ) from the time that the current sense comparator trips to the time at which the control MOSFET actually turns on. We can solve for  $i_{\text{TARGET}}$  knowing there is a delay.

$$i_{\text{TARGET}} = I_F - \frac{\Delta i_L}{2} + \Delta i_D$$

$\Delta i_D$  is the magnitude of current beyond the target current and equal to:

$$\Delta i_D = \left( \frac{V_{\text{OUT}}}{L} \right) t_D$$

Therefore:

$$i_{\text{TARGET}} = I_F - \left( \frac{V_{\text{IN}} - V_{\text{OUT}}}{2L} \right) \times t_{\text{ON}} + \left( \frac{V_{\text{OUT}}}{L} \right) \times t_D$$

The point at which you want the current sense comparator to give the signal to turn on the FET equals:

$$i_{\text{TARGET}} \times R_{\text{SNS}} = 0.20\text{V}$$

Therefore:

$$0.20\text{V} = R_{\text{SNS}} \left( I_F - \left( \frac{V_{\text{IN}} - V_{\text{OUT}}}{2L} \right) \times t_{\text{ON}} + \left( \frac{V_{\text{OUT}}}{L} \right) \times t_D \right)$$

Finally  $R_{\text{SNS}}$  can be calculated.

$$R_{\text{SNS}} = \frac{0.20\text{V}}{\left( I_F - \left( \frac{V_{\text{IN}} - V_{\text{OUT}}}{2L} \right) \times t_{\text{ON}} + \left( \frac{V_{\text{OUT}}}{L} \right) \times t_D \right)}$$

## Standard On-Time Set Calculation

The control MOSFET on-time is variable, and is set with an external resistor  $R_{\text{ON}}$  ( $R_2$  from Figure 1). On-time is governed by the following equation:

$$t_{\text{ON}} = k \times \left( \frac{R_{\text{ON}}}{V_{\text{IN}}} \right)$$

Where

$$k = 1.34 \times 10^{-10}$$

At the conclusion of  $t_{\text{ON}}$  the control MOSFET turns off for a minimum OFF time ( $t_{\text{OFF-MIN}}$ ) of 300 ns, and once  $t_{\text{OFF-MIN}}$  is complete the CS comparator compares  $V_{\text{SNS}}$  and  $V_{\text{REF}}$  again, waiting to begin the next cycle.

The LM3402 / 04 have minimum ON and OFF time limitations. The minimum on time ( $t_{\text{ON}}$ ) is 300 ns, and the minimum allowed off time ( $t_{\text{OFF}}$ ) is 300 ns.

Designing for the highest switching frequency possible means that you will need to know when minimum ON and OFF times are observed.

Minimum OFF time will be seen when the input voltage is at its lowest allowed voltage, and the output voltage is at its maximum voltage (greatest number of series LEDs).

The opposite condition needs to be considered when designing for minimum ON time. Minimum ON time is the point at which the input voltage is at its maximum allowed voltage, and the output voltage is at its lowest value.

## Application Circuit Calculations

To better explain the improvements made to the COT LM3402 / 04 demonstration board, a comparison is shown between the unmodified average output LED current circuit to the improved circuit. Design examples 1 and 2 use two original LM3402 / 04 circuits. The switching frequencies will be maximized to provide a small solution size.

Design example 3 is an improved average current application. Example 3 will be compared against example 2 to illustrate the improvements.

Example 4 will use the same conditions and circuit as example 3, but the switching frequency will be reduced to improve efficiency. The reduced switching frequency can further reduce any variations in average LED current with a wide operating range of series LEDs and input voltages.

### Design Example 1

- $V_{IN} = 48V$  ( $\pm 20\%$ )
  - Driving three HB LEDs with  $V_F = 3.4V$
  - $V_{OUT} = (3 \times 3.4V + 200 \text{ mV}) = 10.4V$
  - $I_F = 500 \text{ mA}$  (typical application)
  - Estimated efficiency = 82%
  - $f_{SW}$  = fast as possible
  - Design for typical application within  $t_{ON}$  and  $t_{OFF}$  limitations
- LED (inductor) ripple current of 10% to 60% is acceptable when driving LEDs. With this much allowed ripple current, you can see that there is no need for an output capacitor. Eliminating the output capacitor is actually desirable. An LED connected to an inductor without a capacitor creates a near perfect current source, and this is what we are trying to create.

In this design we will choose 50% ripple current.

$$\Delta i_L = 500 \text{ mA} \times 0.50 = 250 \text{ mA}$$

$$I_{PEAK} = 500 \text{ mA} + 125 \text{ mA} = 625 \text{ mA}$$

### Calculate $t_{ON}$ , $t_{OFF}$ & $R_{ON}$


From the datasheet there are minimum control MOSFET ON and OFF times that need to be met.

$$t_{OFF} \text{ minimum} = 300 \text{ ns}$$

$$t_{ON} \text{ minimum} = 300 \text{ ns}$$


The minimum ON time will occur when  $V_{IN}$  is at its maximum value. Therefore calculate  $R_{ON}$  at  $V_{IN} = 60V$ , and set  $t_{ON} = 300 \text{ ns}$ .

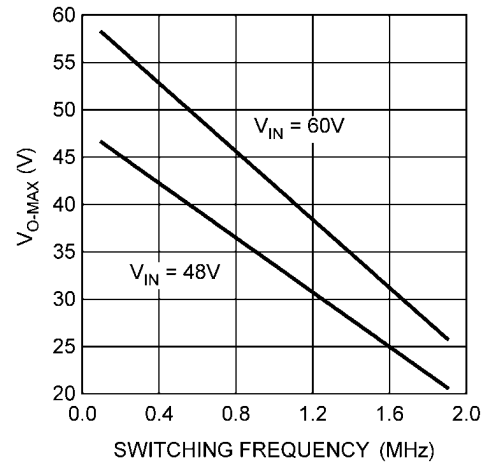A quick guideline for maximum switching frequency allowed versus input and output voltages are shown below in the two graphs (figures 6 & 7).



30061615

FIGURE 6.  $V_{OUT-MAX}$  vs  $f_{SW}$

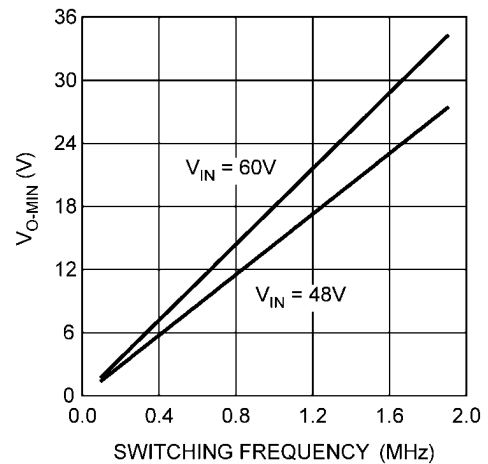

30061616

FIGURE 7.  $V_{OUT-MIN}$  vs  $f_{SW}$

$$t_{ON} = k \times \left( \frac{R_{ON}}{V_{IN}} \right)$$

$$R_{ON} = 135 \text{ k}\Omega \text{ (use standard value of } 137 \text{ k}\Omega)$$

$$t_{ON} = 306 \text{ ns}$$

Check to see if  $t_{OFF}$  minimum is satisfied. This occurs when  $V_{IN}$  is at its minimum value.

At  $V_{IN} = 36V$ , and  $R_{ON} = 137 \text{ k}\Omega$  calculate  $t_{ON}$  from previous equation.

$$t_{ON} = 510 \text{ ns}$$

We know that:

$$D = \frac{V_{OUT}}{V_{IN} \times \eta} = \frac{t_{ON}}{t_{ON} + t_{OFF}}$$

Rearranging the above equation and solving for  $t_{OFF}$  with  $t_{ON}$  set to 510 ns

$$t_{OFF} = t_{ON} \left( \frac{V_{IN} \times \eta}{V_{OUT}} - 1 \right)$$

$t_{OFF} = 938$  ns (satisfied)

**Example 1 ON & OFF Times**

$V_{IN}$ (V)	$V_{OUT}$ (V)	$t_{ON}$	$t_{OFF}$
36	10.4	5.10E-07	9.38E-07
48	10.4	3.82E-07	1.06E-06
60	10.4	3.06E-07	1.14E-06

**Calculate Switching Frequency**

$V_{IN} = 36V, 48$  and  $60V$ .

Substituting equations:

$f_{SW} = 691kHz$  ( $V_{IN} = 36V, 48V, \& 60V$ )

**Calculate Inductor Value**

With 50% ripple at  $V_{IN} = 48V$

- $I_F = 500$  mA
- $\Delta i_L = 250$  mA (target)
- $L = 57 \mu H$  (68  $\mu H$  standard value)

Calculate  $\Delta i$  for  $V_{IN} = 36V, 48V,$  and  $60V$  with  $L = 68 \mu H$

**Example 1 Ripple Current**

$V_{IN}$ (V)	$V_{OUT}$ (V)	$\Delta i_L$ (A)
36	10.4	0.192
48	10.4	0.211
60	10.4	0.223

**Calculate  $R_{SNS}$**

Calculate  $R_{SNS}$  at  $V_{IN}$  typical (48V), and average LED current ( $I_F$ ) set to 500 mA.

- $I_F = 500$  mA
- $V_{IN} = 48V$
- $V_{OUT} = 10.4V$
- $L = 68 \mu H$
- $t_D = 220$  ns
- $t_{ON} = 382$  ns

Using equations from the COT Overview section, calculate  $R_{SNS}$ .

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{V_{IN} - V_{OUT}}{2L} \right) \times t_{ON} + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

Or:

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{V_{IN} - V_{OUT}}{2L} \right) \left( \frac{k \times R_{ON}}{V_{IN}} \right) + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

Therefore:  $R_{SNS} = 467$  m $\Omega$


**Calculate Average LED current ( $I_F$ )**

Calculate average current through the LEDs for  $V_{IN} = 36V$  and  $60V$ .

$$I_F = \frac{0.20V}{R_{SNS}} + \left( \frac{V_{IN} - V_{OUT}}{2L} \right) (t_{ON}) - \left( \frac{V_{OUT} \times t_D}{L} \right)$$

**Example 1 Average LED Current**

$V_{IN}$ (V)	$V_{OUT}$ (V)	$I_F$ (A)
36	10.4	0.490
48	10.4	0.500
60	10.4	0.506

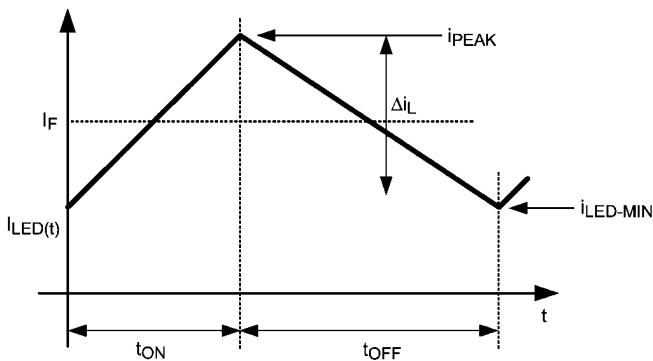

30061623

**FIGURE 8. Inductor Current Waveform**

**Design Example 2**

Design example 2 demonstrates a design if a single Bill of Materials (Bom) is desired over many different applications (number of series LEDs,  $V_{IN}$ ,  $V_{OUT}$  etc).

- $V_{IN} = 48V$  ( $\pm 20\%$ )
- Driving 3, 4, or 5 HB LEDs with  $V_F = 3.4V$
- $I_F = 500$  mA (typical application)
- Estimated efficiency = 82%
- $f_{SW}$  = fast as possible
- Design for typical application within  $t_{ON}$  and  $t_{OFF}$  limitations

The inductor,  $R_{ON}$  resistor, and the  $R_{SNS}$  resistor is calculated for a typical or average design.

- $V_{OUT} = 3 \times 3.4V + 200$  mV = 10.4V
- $V_{OUT} = 4 \times 3.4V + 200$  mV = 13.8V
- $V_{OUT} = 5 \times 3.4V + 200$  mV = 17.2V

**Calculate  $t_{ON}$ ,  $t_{OFF}$  &  $R_{ON}$** 

In this design we will maximize the switching frequency so that we can reduce the overall size of the design. In a later design, a slower switching frequency is utilized to maximize efficiency. If the design is to use the highest possible switching frequency, you must ensure that the minimum on and off times are adhered to.

Minimum on time occurs when  $V_{IN}$  is at its maximum value, and  $V_{OUT}$  is at its lowest value.

Calculate  $R_{ON}$  at  $V_{IN} = 60V$ ,  $V_{OUT} = 10.4V$ , and set  $t_{ON} = 300$  ns:

$$t_{ON} = k \times \left( \frac{R_{ON}}{V_{IN}} \right)$$

$R_{ON} = 137$  k $\Omega$ ,  $t_{ON} = 306$  ns

Check to see if  $t_{OFF}$  minimum is satisfied:

$t_{OFF}$  minimum occurs when  $V_{IN}$  is at its lowest value, and  $V_{OUT}$  is at its maximum value.

At  $V_{IN} = 36V$ ,  $V_{OUT} = 17.2V$ , and  $R_{ON} = 137$  k $\Omega$  calculate  $t_{ON}$  from the above equation:

$t_{ON} = 510$  ns

$$\frac{V_{IN} \times \eta}{V_{OUT}} = \frac{t_{ON}}{t_{ON} + t_{OFF}}$$

Rearrange the above equation and solve for  $t_{OFF}$  with  $t_{ON}$  set to 510 ns

$$t_{OFF} = t_{ON} \left( \frac{V_{IN} \times \eta}{V_{OUT}} - 1 \right)$$

$t_{OFF} = 365$  ns (satisfied)

**Example 2 On & Off Time**

<b>Three Series LEDs</b>				
$V_{IN}$ (V)	$V_{OUT}$ (V)	$R_{ON}$	$t_{ON}$	$t_{OFF}$
36	10.4	137 k $\Omega$	5.10E-07	9.38E-07
48	10.4	137 k $\Omega$	3.82E-07	1.06E-06
60	10.4	137 k $\Omega$	3.06E-07	1.14E-06
<b>Four Series LEDs</b>				
36	13.8	137 k $\Omega$	5.10E-07	5.81E-07
48	13.8	137 k $\Omega$	3.82E-07	7.08E-07
60	13.8	137 k $\Omega$	3.06E-07	7.85E-07
<b>Five Series LEDs</b>				
36	17.2	137 k $\Omega$	5.10E-07	3.65E-07
48	17.2	137 k $\Omega$	3.82E-07	4.93E-07
60	17.2	137 k $\Omega$	3.06E-07	5.69E-07

**Calculate Switching Frequency**

The switching frequency will only change with output voltage.

$$f_{SW} = \frac{V_{OUT}}{V_{IN} \times \eta \times t_{ON}}$$

Substituting equations:

$$f_{SW} = \frac{V_{OUT}}{\eta \times k \times R_{ON}}$$

Or:

$$f_{SW} = \frac{1}{t_{ON} + t_{OFF}}$$

- $f_{SW} = 691$  kHz ( $V_{OUT} = 10.4V$ )
- $f_{SW} = 916$  kHz ( $V_{OUT} = 13.8V$ )
- $f_{SW} = 1.14$  MHz ( $V_{OUT} = 17.2V$ )

**Calculate Inductor Value**

$$L = \left( \frac{V_{IN} - V_{OUT}}{\Delta i} \right) \times t_{ON}$$

With 50% ripple at  $V_{IN} = 48V$ , and  $V_{OUT} = 10.4V$

- $I_{AVG} = 500$  mA
- $\Delta i_L = 250$  mA (target)
- $L = 53$   $\mu$ H (68  $\mu$ H standard value)

Calculate  $\Delta i$  for  $V_{IN} = 36V$ , 48V, & 60V with  $L = 68$   $\mu$ H.

## Example 2 Ripple Current

V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)	Δi <sub>L</sub> (A)
<b>Three Series LEDs</b>		
36	10.4	0.192
48	10.4	0.211
60	10.4	0.223
<b>Four Series LEDs</b>		
36	13.8	0.166
48	13.8	0.192
60	13.8	0.208
<b>Four Series LEDs</b>		
36	17.2	0.141
48	17.2	0.173
60	17.2	0.193

Calculate R<sub>SNS</sub>

Calculate R<sub>SNS</sub> at V<sub>IN</sub> typical (48V), with four series LEDs (13.8V = V<sub>OUT</sub>), and average LED current (I<sub>F</sub>) set to 500 mA.

- I<sub>F</sub> = 500 mA
- V<sub>IN</sub> = 48V
- V<sub>OUT</sub> = 13.8V
- L = 68 μH
- t<sub>D</sub> = 220 ns
- t<sub>ON</sub> = 382 ns

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{V_{IN} - V_{OUT}}{2L} \right) \times t_{ON} + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

$$R_{SNS} = 446 \text{ m}\Omega$$

## Calculate Average Current through LED

All combinations of V<sub>IN</sub>, V<sub>OUT</sub> with R<sub>SNS</sub> = 446 mΩ

$$I_F = \frac{0.20V}{R_{SNS}} + \left( \frac{V_{IN} - V_{OUT}}{2L} \right) (t_{ON}) - \left( \frac{V_{OUT} \times t_D}{L} \right)$$

## Example 2 Average LED Current

V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)	I <sub>F</sub> (A)
<b>Three Series LEDs</b>		
36	10.4	0.511
48	10.4	0.521
60	10.4	0.526
<b>Four Series LEDs</b>		
36	13.8	0.487
48	13.8	0.500
60	13.8	0.508
<b>Five Series LEDs</b>		
36	17.2	0.463
48	17.2	0.479
60	17.2	0.489

In this application you can see that there is a difference of 63 mA between the low and high of the average LED current.

## Modified COT Application Circuit

With the addition of one pnp transistor and one resistor (Q1 and R3) the average current through the LEDs can be made to be more constant over input and output voltage variations. Refer to page one figure 1. Resistor R<sub>ON</sub> (R2) and Q1 turn the t<sub>ON</sub> equation into:

$$t_{ON} = k \times \left( \frac{R_{ON}}{V_{IN} - V_{OUT}} \right)$$

Ignore the PNP transistor's V<sub>BE</sub> voltage drop.

Design to the same criteria as the previous example with the improved application and compare results.

# Modified Application Circuit Design

## Example 3

### Design Example 1

- $V_{IN} = 48V (\pm 20\%)$
- Driving 3, 4, or 5 HB LEDs with  $V_F = 3.4V$
- $I_F = 500\text{ mA}$  (typical application)
- Estimated efficiency = 82%
- $f_{SW} =$  fast as possible
- Design for typical application within  $t_{ON}$  and  $t_{OFF}$  limitations

The inductor,  $R_{ON}$  resistor, and the  $R_{SNS}$  resistor are calculated for a typical or average design.

- $V_{OUT} = 3 \times 3.4V + 200\text{ mV} = 10.4V$
- $V_{OUT} = 4 \times 3.4V + 200\text{ mV} = 13.8V$
- $V_{OUT} = 5 \times 3.4V + 200\text{ mV} = 17.2V$

### Calculate $t_{ON}$ , $t_{OFF}$ & $R_{ON}$

Minimum ON time occurs when  $V_{IN}$  is at its maximum value, and  $V_{OUT}$  is at its lowest value.

Calculate  $R_{ON}$  at  $V_{IN} = 60V$ ,  $V_{OUT} = 10.4V$ , and set  $t_{ON} = 300\text{ ns}$ :

$$R_{ON} = t_{ON} \left( \frac{V_{IN} - V_{OUT}}{k} \right)$$

$R_{ON} = 111\text{ k}\Omega$  (113 k $\Omega$ )  $t_{ON} = 306\text{ ns}$

Check to see if  $t_{OFF}$  minimum is satisfied.

At  $V_{IN} = 36V$ ,  $V_{OUT} = 17.2V$ , and  $R_{ON} = 113\text{ k}\Omega$  calculate  $t_{ON}$ :

$t_{ON} = 806\text{ ns}$

$$t_{OFF} = t_{ON} \left( \frac{V_{IN} \times \eta}{V_{OUT}} - 1 \right)$$

$t_{OFF} = 577\text{ ns}$  (satisfied)

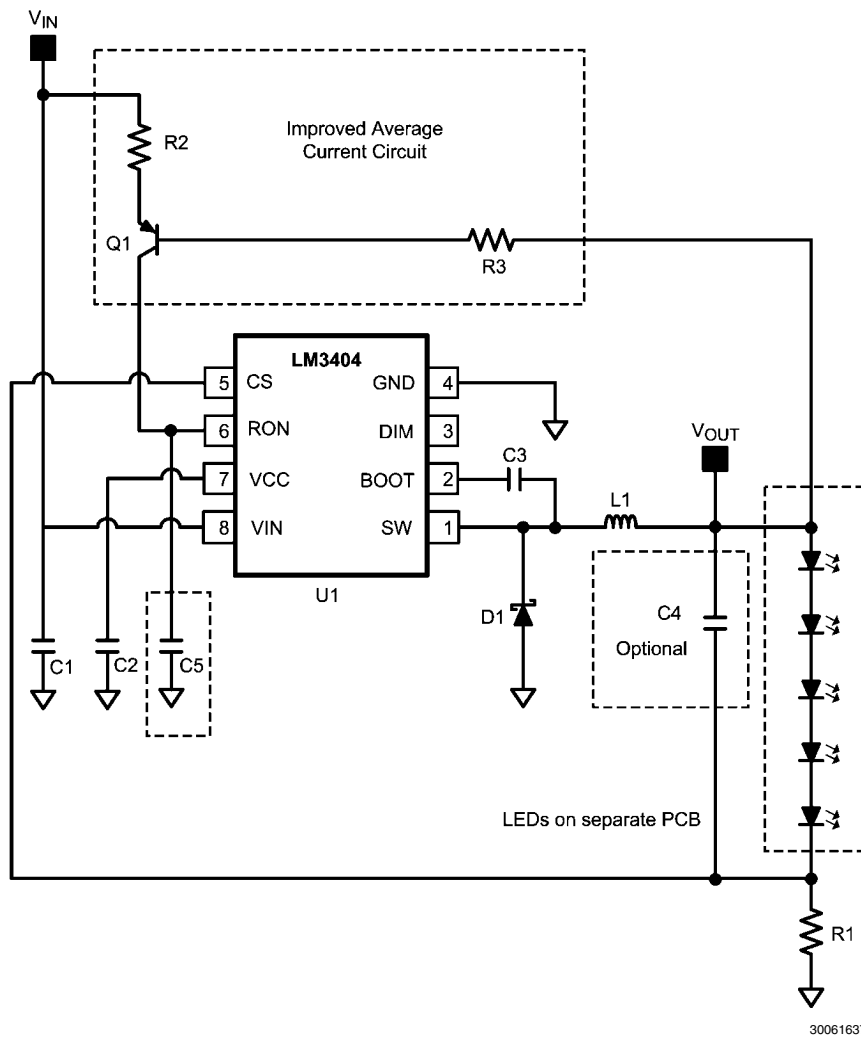


FIGURE 9. Improved Average LED Current Application Circuit

30061637



### Example 3 On & Off Times

Three Series LEDs				
V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)	R <sub>ON</sub>	t <sub>ON</sub>	t <sub>OFF</sub>
36	10.4	113 kΩ	5.92E-07	1.09E-07
48	10.4	113 kΩ	4.03E-07	1.12E-06
60	10.4	113 kΩ	<b>3.06E-07</b>	1.14E-06
Four Series LEDs				
36	13.8	113 kΩ	6.83E-07	7.78E-07
48	13.8	113 kΩ	4.43E-07	8.21E-07
60	13.8	113 kΩ	3.28E-07	8.41E-07
Five Series LEDs				
36	17.2	113 kΩ	8.06E-07	<b>5.77E-07</b>
48	17.2	113 kΩ	4.92E-07	6.34E-07
60	17.2	113 kΩ	3.54E-07	6.59E-07

#### Calculate Switching Frequency

$$f_{SW} = \frac{V_{OUT}}{V_{IN} \times \eta \times t_{ON}}$$

Or:

$$f_{SW} = \frac{1}{t_{ON} + t_{OFF}}$$

#### Example 3 Switching Frequency

V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)	f <sub>SW</sub> (kHz)
Three Series LEDs		
36	10.4	595
48	10.4	656
60	10.4	692
Four Series LEDs		
36	13.8	685
48	13.8	<b>791</b>
60	13.8	855
Five Series LEDs		
36	17.2	723
48	17.2	888
60	17.2	987

#### Calculate Inductor Value

$$L = \left( \frac{V_{IN} - V_{OUT}}{\Delta i} \right) \times t_{ON}$$

$$t_{ON} = k \times \left( \frac{R_{ON}}{V_{IN} - V_{OUT}} \right)$$

Therefore:

$$L = \left( \frac{R_{ON}}{\Delta i} \right) \times k$$

You can quickly see one benefit of the modified circuit. The improved circuit eliminates the input and output voltage variation on RMS current.

- I<sub>F</sub> = 500 mA (typical application)
- Δi<sub>L</sub> = 250 mA (target)
- R<sub>ON</sub> = 113 kΩ
- L = 59 μH (68 μH standard value)
- Δi<sub>L</sub> = 223 mA (L = 68 μH all combinations)

#### Calculate R<sub>SNS</sub>

Original R<sub>SNS</sub> equation:

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{V_{IN} - V_{OUT}}{2L} \right) \times t_{ON} + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

Substitute improved circuit t<sub>ON</sub> calculation:

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{V_{IN} - V_{OUT}}{2L} \right) \left( k \times \frac{R_{ON}}{V_{IN} - V_{OUT}} \right) + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

Simplified:

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{k \times R_{ON}}{2L} \right) + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

Typical Application:

- V<sub>OUT</sub> = 13.8V
- I<sub>F</sub> = 500 mA
- R<sub>ON</sub> = 113 kΩ
- L = 68 μH
- t<sub>D</sub> = 220 ns

$$R_{SNS} = 462 \text{ m}\Omega$$

This equation shows that only variations in V<sub>OUT</sub> will affect the average current over the entire application range. These variations should be very minor even with large variations in output voltage.

#### Calculate Average Current through LED

Modified application circuit average forward current equation.

$$I_F = \frac{0.20V}{R_{SNS}} + \left( \frac{V_{IN} - V_{OUT}}{2L} \right) \left( \frac{k \times R_{ON}}{V_{IN} - V_{OUT}} \right) - \left( \frac{V_{OUT} \times t_D}{L} \right)$$

Simplified:

$$I_F = \frac{0.20V}{R_{SNS}} + \left( \frac{k \times R_{ON}}{2L} \right) - \left( \frac{V_{OUT} \times t_D}{L} \right)$$

## Example 3 Average LED Current

$V_{IN}$ (V)	$V_{OUT}$ (V)	$I_F$ (A)
<b>Three Series LEDs</b>		
36	10.4	0.511
48	10.4	0.511
60	10.4	0.511
<b>Four Series LEDs</b>		
36	13.8	0.500
48	13.8	0.500

$V_{IN}$ (V)	$V_{OUT}$ (V)	$I_F$ (A)
<b>Three Series LEDs</b>		
60	13.8	0.500
<b>Five Series LEDs</b>		
36	17.2	0.489
48	17.2	0.489
60	17.2	0.489

In this application you can see that there is a difference of **22 mA** between the low and high of the average LED current.

## Modified Application Circuit Design

### Example 4

- $V_{IN} = 48V (\pm 20\%)$
- Driving 3, 4, or 5 HB LEDs with  $V_F = 3.4V$
- $I_F = 500 \text{ mA}$  (typical application)
- Estimated efficiency = 82%
- $f_{SW} = 500 \text{ kHz}$  (typ app)

The inductor,  $R_{ON}$  resistor, and the  $R_{SNS}$  resistor are calculated for a typical or average design.

- $V_{OUT} = 3 \times 3.4V + 200 \text{ mV} = 10.4V$
- $V_{OUT} = 4 \times 3.4V + 200 \text{ mV} = 13.8V$
- $V_{OUT} = 5 \times 3.4V + 200 \text{ mV} = 17.2V$

Reduce switching frequency for the typical application to about 500 kHz to increase efficiency.

#### Calculate $t_{ON}$ , $t_{OFF}$ & $R_{ON}$

$$t_{ON} = \left( \frac{V_{OUT}}{V_{IN} \times \eta} \right) \left( \frac{1}{f_{SW}} \right)$$

- $V_{OUT} = 13.8V$
- $V_{IN} = 48V$
- $I_F = 500 \text{ mA}$
- $t_D = 220 \text{ ns}$
- $\eta = 0.85$
- $f_{SW} = 500 \text{ kHz}$

$$t_{ON} \approx 705 \text{ ns}$$

$$R_{ON} = \left( \frac{t_{ON}}{k} \right) (V_{IN} - V_{OUT})$$

$R_{ON} \approx 179 \text{ k}\Omega$  (use standard value of 182  $\text{k}\Omega$ )

#### Calculate Inductor Value

$$L = \left( \frac{R_{ON}}{\Delta i} \right) \times k$$

- $I_F = 500 \text{ mA}$
- $\Delta i_L = 250 \text{ mA}$  (target)
- $R_{ON} = 182 \text{ k}\Omega$
- $L = 100 \text{ }\mu\text{H}$

Calculate  $\Delta i_L$  with  $L = 100 \text{ }\mu\text{H}$  ( $V_{IN} = 48V$ ,  $V_{OUT} = 13.8V$ )

$\Delta i_L = 241 \text{ mA}$  (all combinations)

#### Calculate Switching Frequency

$$f_{SW} = \frac{V_{OUT}}{V_{IN} \times \eta \times t_{ON}}$$

Or:

$$f_{SW} = \frac{1}{t_{ON} + t_{OFF}}$$

#### Example 4 Switching Frequency

$V_{IN}$ (V)	$V_{OUT}$ (V)	$f_{SW}$ (kHz)
<b>Three Series LEDs</b>		
36	10.4	374
48	10.4	412

$V_{IN}$ (V)	$V_{OUT}$ (V)	$f_{SW}$ (kHz)
<b>Three Series LEDs</b>		
60	10.4	435
<b>Four Series LEDs</b>		
36	13.8	430
48	13.8	497
60	13.8	537
<b>Five Series LEDs</b>		
36	17.2	454
48	17.2	558
60	17.2	620

#### Calculate $R_{SNS}$

$$R_{SNS} = \frac{0.20V}{(I_F) - \left( \frac{k \times R_{ON}}{2L} \right) + \left( \frac{V_{OUT} \times t_D}{L} \right)}$$

- $V_{OUT} = 13.8V$
- $V_{IN} = 48V$
- $I_F = 500 \text{ mA}$
- $t_D = 220 \text{ ns}$
- $\eta = 0.85$
- $L = 100 \text{ }\mu\text{H}$

$$R_{SNS} = 488 \text{ m}\Omega$$

#### Calculate Average Current through LED

$$I_F = \frac{0.20V}{R_{SNS}} + \left( \frac{k \times R_{ON}}{2L} \right) - \left( \frac{V_{OUT} \times t_D}{L} \right)$$

#### Example 4 Average LED Current

$V_{IN}$ (V)	$V_{OUT}$ (V)	$I_F$ (A)
<b>Three Series LEDs</b>		
36	10.4	0.507
48	10.4	0.507
60	10.4	0.507
<b>Four Series LEDs</b>		
36	13.8	0.500
48	13.8	<b>0.500</b>
60	13.8	0.500
<b>Five Series LEDs</b>		
36	17.2	0.493
48	17.2	0.493
60	17.2	0.493

In the reduced frequency application you can see that there is a difference of 14 mA between the low and high of the average current.

If the original  $t_{ON}$  circuit was used (no PNP transistor) with the switching frequency centered around 500 kHz the difference between the high and low values would be about **67 mA**.

## Dimming


The DIM pin of the LM3402/04 is a TTL compatible input for low frequency pulse width modulation (PWM) dimming of the LED current. Depending on the application, a contrast ratio greater than what the LM3402/04 internal DIM circuitry can provide might be needed. This demonstration board comes with external circuitry that allows for dimming contrast ratios greater than 50k:1

### LM3402 / 04 DIM Pin Operation

To fully enable and disable the LM3402 / 04, the PWM signal should have a maximum logic low level of 0.8V and a minimum logic high level of 2.2V. Dimming frequency,  $f_{DIM}$ , and duty cycle,  $D_{DIM}$ , are limited by the LED current rise time and fall time and the delay from activation of the DIM pin to the response of the internal power MOSFET. In general,  $f_{DIM}$

should be at least one order of magnitude lower than the steady state switching frequency in order to prevent aliasing. Refer to figure 10 for illustrations. The interval  $t_D$  represents the delay from a logic high at the DIM pin to the onset of the output current. The quantities  $t_{SU}$  and  $t_{SD}$  represent the time needed for the LED current to slew up to steady state and slew down to zero, respectively.

As an example, assume a DIM duty cycle  $D_{DIM}$  equal to 100% (always on) and the circuit delivers 500mA of current through the LED string. At  $D_{DIM}$  equal to 50% you would like exactly 1/2 of 500 mA of current through your LED string (250 mA). This could only be possible if there were no delays ( $t_D$ ) between the on/off DIM signal and the on/off of the LED current. The rise and fall times ( $t_{SU}$  and  $t_{SD}$ ) of the LED current would also need to be eliminated. If we can reduce these times, the linearity between the PWM signal and the average current will be realized.

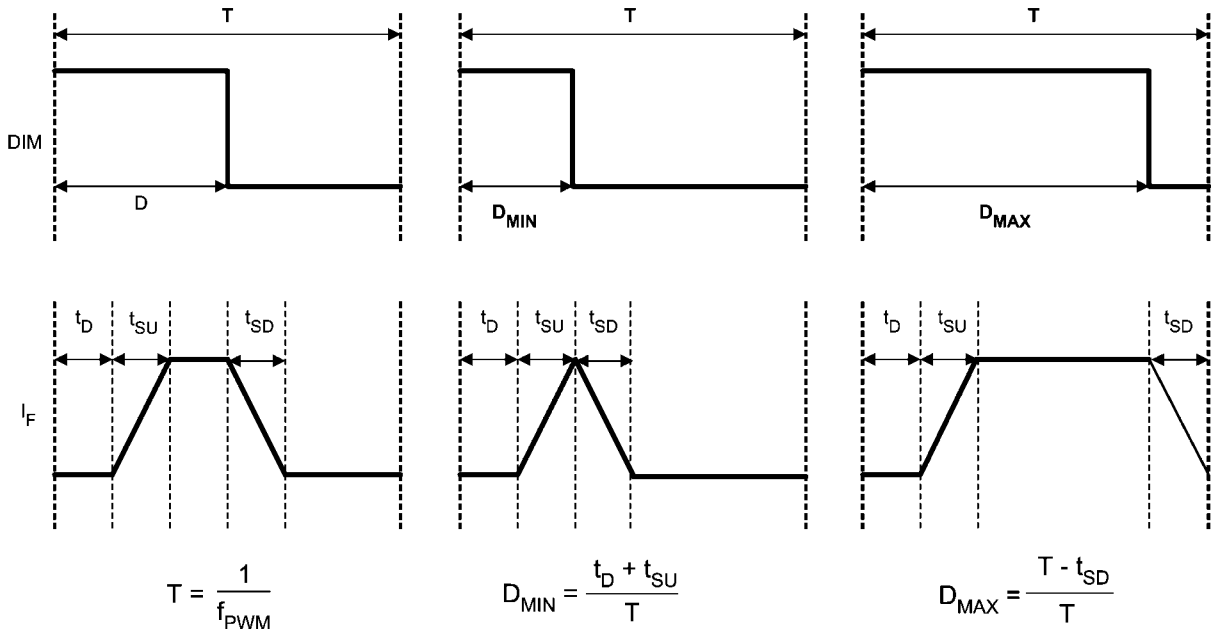


30061652

FIGURE 10. Contrast Ratio Definitions
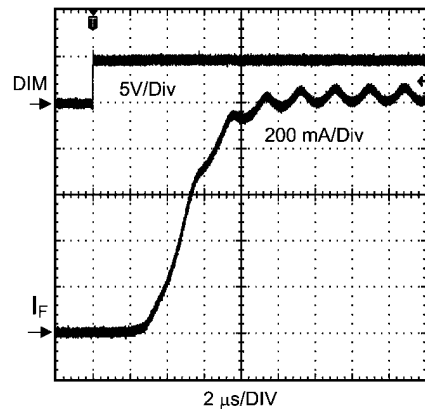
### Contrast Ratio Definition

Contrast Ratio (CR) =  $1/D_{MIN}$   
 $D_{MIN} = (t_D + t_{SU}) \times f_{DIM}$




30061653

FIGURE 11.  $t_D$  &  $t_{SU}$  (DIM Pin)
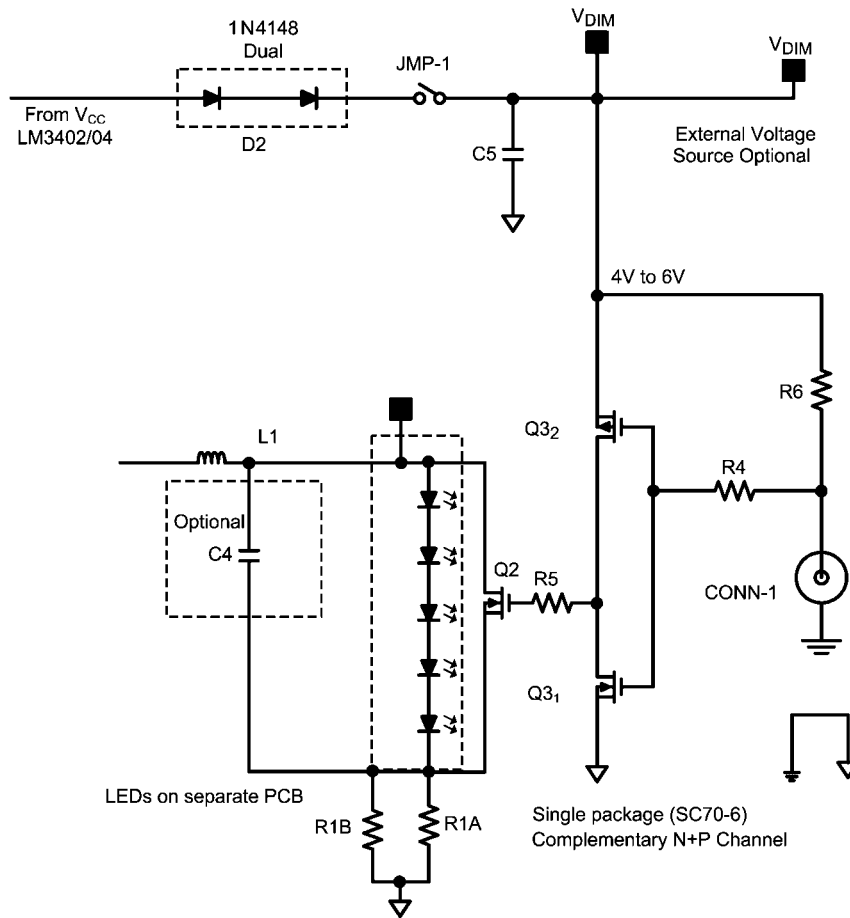
## External MOSFET Dimming and Contrast Ratio


Refer to figure 12. MOSFET Q2 and its drive circuitry are provided on the demonstration PCB. When MOSFET Q2 is turned on, it shorts LED+ to LED-, therefore redirecting the

inductor current from the LED string to the shunt MOSFET. The LM3402 / 04 is never turned off, and therefore become a perfect current source by providing continuous current to the output through the inductor (L1). A buck converter with an external shunt MOSFET is the ideal circuit for delivering the highest possible contrast ratio. Refer to figures 13-15 for typical delays and rise time for external MOSFET dimming.




30061654

FIGURE 12.

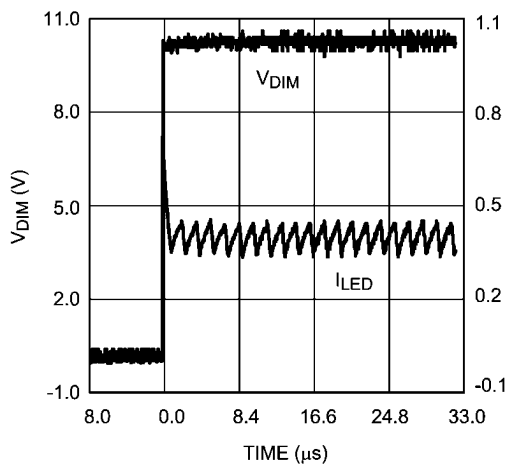


30061655

FIGURE 13.  $V_{IN} = 24V$ , 3 series LEDs @ 400mA

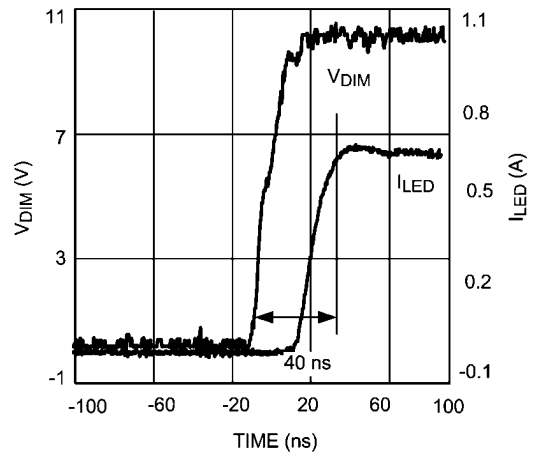

30061656

FIGURE 14.  $t_D + t_{SU}$  Graph

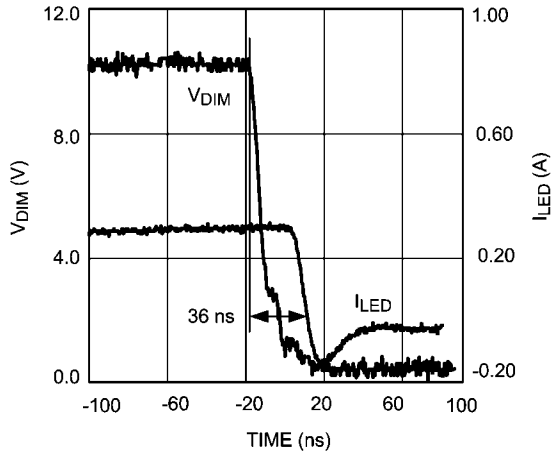

30061657

FIGURE 15.  $t_D + t_{SD}$  Graph

### Fast Dimming + Improved Average Current Circuit

Using both the Improved Average LED current circuit and the external MOSFET fast dimming circuit together has additional benefits. If  $R_{ON}$  and the converter's switching frequency ( $f_{SW}$ ) is determined and set with the improved average LED current circuit, the switching frequency will decrease once  $V_{OUT}$  is shorted during fast dimming. With MOSFET Q2 on,  $V_{OUT}$  is equal to  $V_{FB}$  (200 mV). The  $t_{ON}$  equation then becomes almost identical to the original unmodified circuit equation.

Setting  $t_{ON}$  and  $R_{ON}$ :

$$t_{ON} = k \times \left( \frac{R_{ON}}{V_{IN} - V_{OUT}} \right)$$

$t_{ON}$  equation becomes:

$$t_{ON} = k \times \left( \frac{R_{ON}}{V_{IN} - 0.2V} \right)$$

when Q2 shunt MOSFET is on during fast dimming.

$t_{OFF}$  equation during normal operation is:


$$t_{OFF} = t_{ON} \left( \frac{V_{IN} \times \eta}{V_{OUT}} - 1 \right)$$

$t_{OFF}$  equation then becomes:

$$t_{OFF} = t_{ON} \left( \frac{V_{IN} \times \eta}{0.2V} - 1 \right)$$

when Q2 shunt MOSFET is OFF during fast dimming.

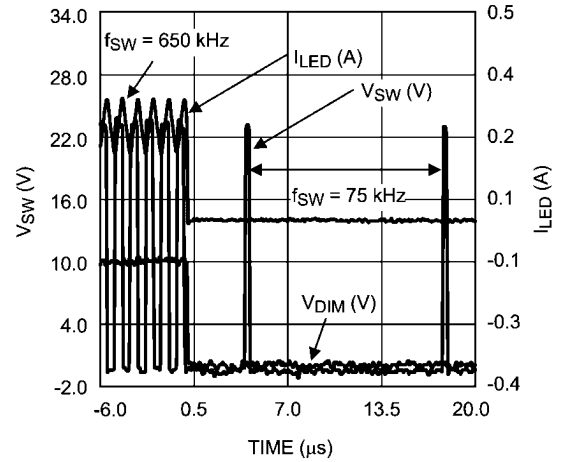This is an added benefit due to the fact that  $t_{OFF}$  is greatly increased, and therefore the switching frequency is decreased, which leads to improved efficiency (see figure 16). Inductor L1 still remains charged, and as soon as Q2 turns off current flows through the LED string.




30061662

FIGURE 16. Improved Avg  $I_{LED}$  Circuit + Fast Dimming
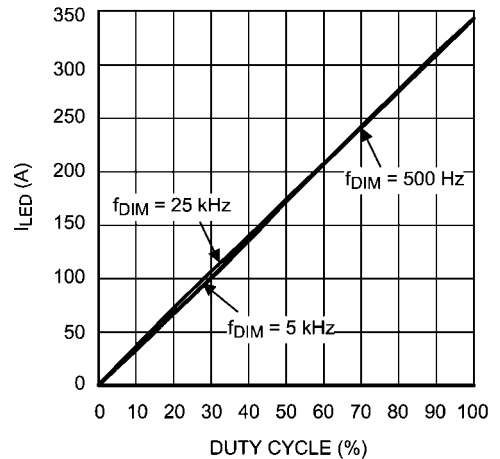
### Linearity with Fast Dimming


Once the delays and rise/fall times have been greatly reduced, linear average current vs. duty cycle ( $D_{DIM}$ ) can be achieved at very high dimming frequencies ( $f_{DIM}$ ) (see figure 17).



30061663

FIGURE 17. Linearity with Fast Dimming
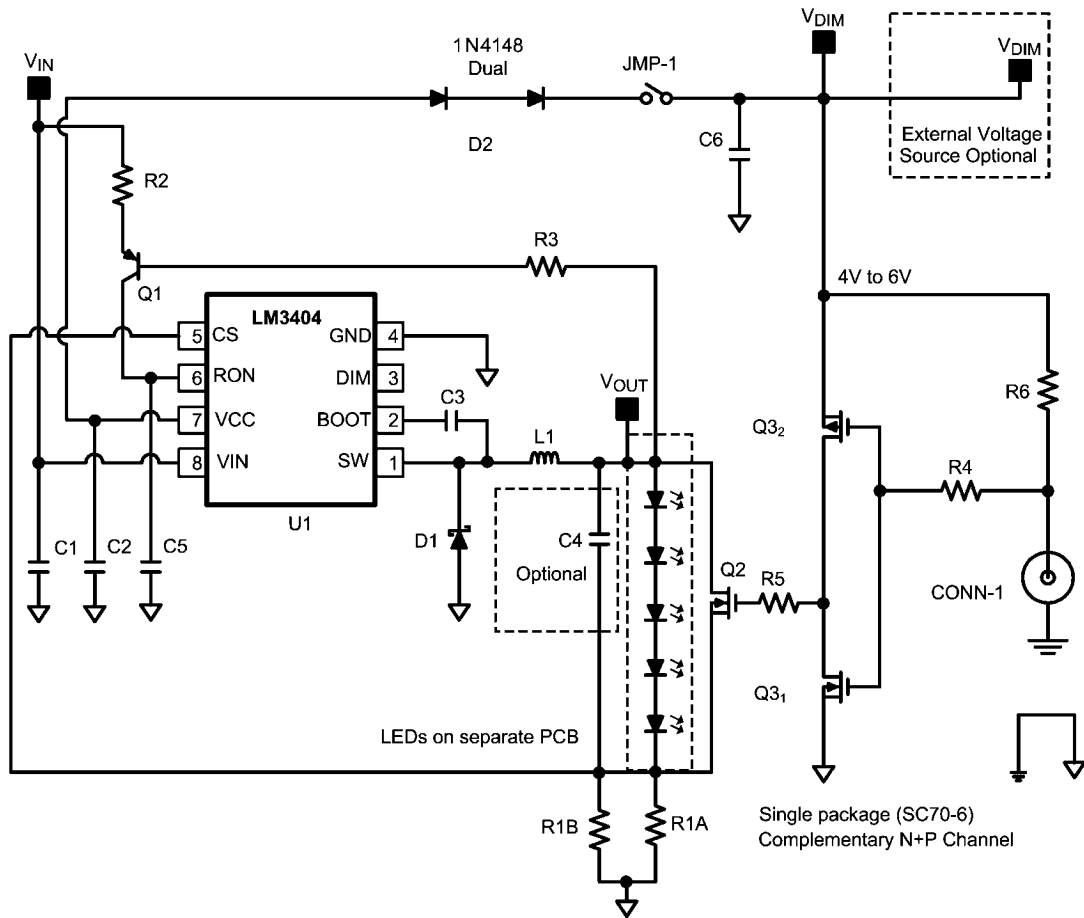
# LM3402 Improved ILED Average & Fast Dimming Demonstration Board



$V_{IN} = 9V \text{ to } 18V, I_{LED} = 500 \text{ mA}, 3 \times 3.4V \text{ White LED Strings } (f_{sw} \approx 750 \text{ kHz})$


30061601

## Bill of Materials

Part ID	Part Value	Mfg	Part Number
U1	0.5A Buck LED Driver PSOP pkg	NSC	LM3402
C1, Input Cap	10 $\mu$ F, 25V, X5R	TDK	C3225X5R1E106M
C2, C6 Cap	1 $\mu$ F, 16V, X5R	TDK	C1608X5R1C105M
C3, V <sub>BOOST</sub> Cap	0.1 $\mu$ F, X5R	TDK	C1608X5R1H104M
C4 Output Cap	10 $\mu$ F, 25V, X5R (Optional)	TDK	C3225X5R1E106M
C5, V <sub>RON</sub> Cap	0.01 $\mu$ F, X5R	TDK	C1608X5R1H103M
D1, Catch Diode	0.5V <sub>f</sub> Schottky 2A, 30V <sub>R</sub>	Diodes INC	B230
D2	Dual SMT small signal	Diodes INC	BAV199
L1	33 $\mu$ H	CoilCraft	D01813H-333
R1A, R1B	1 $\Omega$ 1% 0.25W 1206	Panasonic	ERJ-8RQF1R0V
R2	64.9 k $\Omega$ 1%	Vishay	CRCW08056492F
R3	1.0 k $\Omega$ , 1%	Vishay	CRCW08051001F
R4, R5	1 $\Omega$ , 1%	Vishay	CRCW08051R00F
R6	10 k $\Omega$ , 1%	Vishay	CRCW08051002F
Q1	SOT23 PNP	Diodes INC	MMBT3906
Q2	SOT23-6 N-CH 2.4A, 20V	ZETEX	ZXM2A01E6CT
Q3	SC70-6, P + N Channel	Vishay	Si1539DL
Test Points	Connector	Keystone	1502-2
VIN, GND, LED+, LED-	Connector	Keystone	575-8
JMP-1	Jumper	Molex	22-28-4023



# Layout

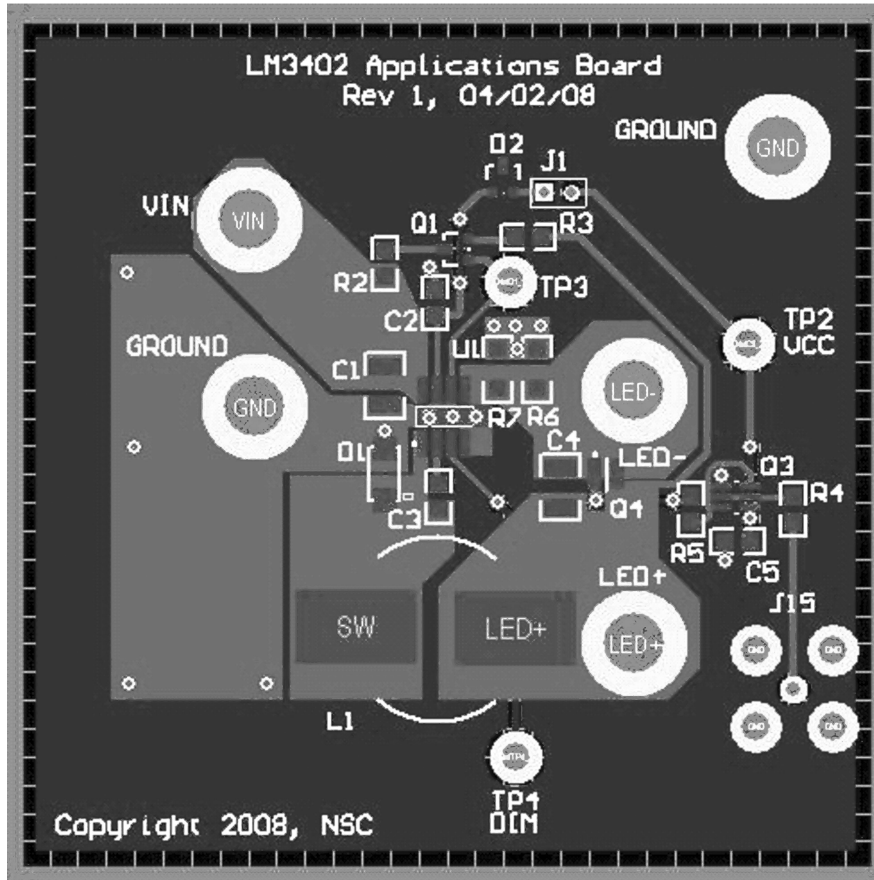

30061665

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	Analog University	<a href="http://www.national.com/AU">www.national.com/AU</a>
Clock Conditioners	<a href="http://www.national.com/timing">www.national.com/timing</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Data Converters	<a href="http://www.national.com/adc">www.national.com/adc</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
Displays	<a href="http://www.national.com/displays">www.national.com/displays</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Ethernet	<a href="http://www.national.com/ethernet">www.national.com/ethernet</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Feedback	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>		
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>		
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>		
PowerWise	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>		
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>		
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>		
Wireless (PLL/VCO)	<a href="http://www.national.com/wireless">www.national.com/wireless</a>		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.


**LIFE SUPPORT POLICY**

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation  
 For the most current product information visit us at [www.national.com](http://www.national.com)

 <p><b>National Semiconductor Americas Technical Support Center</b>                  Email: <a href="mailto:support@nsc.com">support@nsc.com</a>                  Tel: 1-800-272-9959</p>	<p><b>National Semiconductor Europe Technical Support Center</b>                  Email: <a href="mailto:europe.support@nsc.com">europe.support@nsc.com</a>                  German Tel: +49 (0) 180 5010 771                  English Tel: +44 (0) 870 850 4288</p>	<p><b>National Semiconductor Asia Pacific Technical Support Center</b>                  Email: <a href="mailto:ap.support@nsc.com">ap.support@nsc.com</a></p>	<p><b>National Semiconductor Japan Technical Support Center</b>                  Email: <a href="mailto:jpn.feedback@nsc.com">jpn.feedback@nsc.com</a></p>
--	--	---	--