

LED Drivers for General Illumination



Presenter:

- **Chris Richardson**
- **Systems Applications Engineer, Lighting**
- **Europe**

Agenda

- **What is “General Illumination”?**
- **3 Pieces of the Puzzle**
- **Challenges in General Illumination**
- **Arraying your LEDs**
 - All in series
 - Series-parallel
- **AC to CC (Constant Current)**
- **DC Bus with Multiple DC-DC LED Drivers**
 - Buck is Best
 - Boost for Long Strings
 - Buck-boost: when all else fails!

What General Illumination is:

Non-portable lighting, usually running from line power (AC mains)

Streetlighting



High Power Wide Area




Interior Lighting



Emergency, Downlight

Exterior Lighting

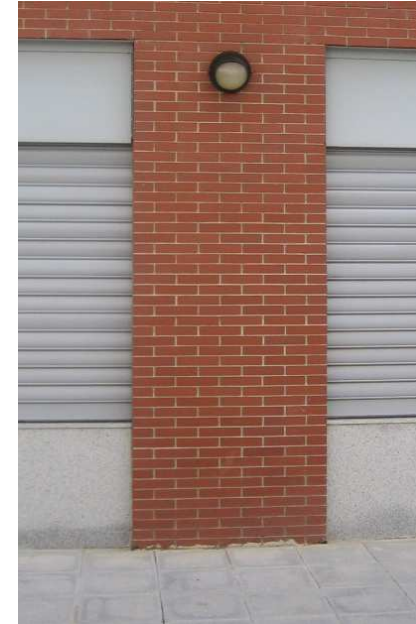

Accent




Three Pieces of the Puzzle


- Thermal is critical. Good designs integrate heat-sinking into the structure of the lamp



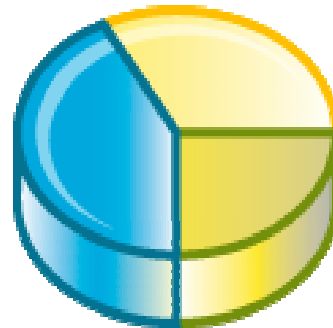- Optical – also critical, must be integrated into the mechanical design of the lamp




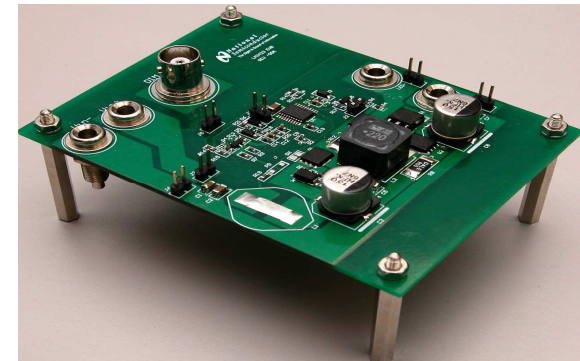- Electrical Drive: often an afterthought (like most power supplies)



Why use a Driver?

- Why not a resistor?

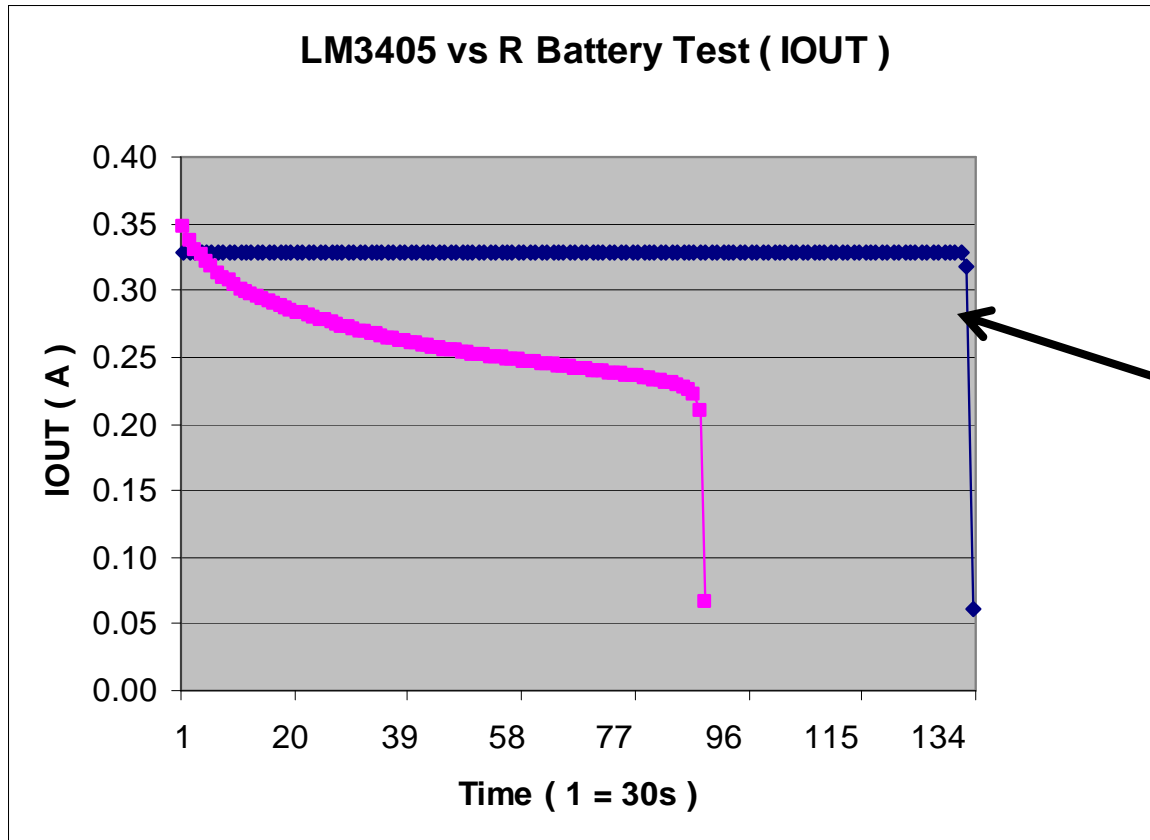

- Drivers are regulated power supplies
- Output current is regulated
- Output Power can also be regulated
- Switching regulators get the most from the battery!

BLUE = LM3405 LED Driver

PURPLE = Series Resistor




Challenges of General Illumination with LEDs




Many Opportunities, Few Standards

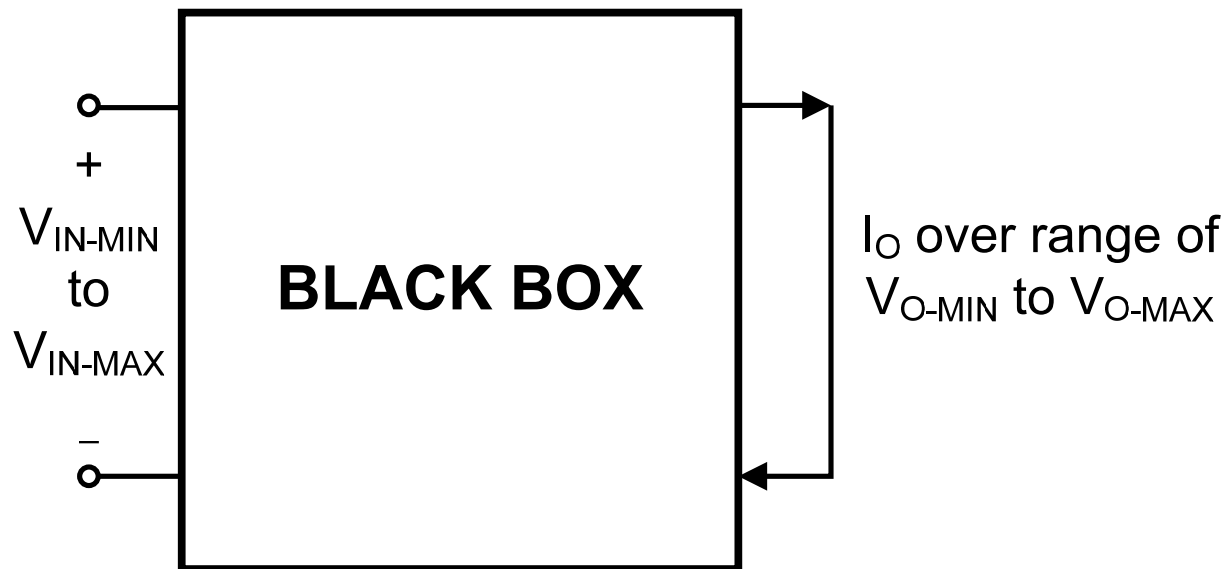- LED lighting is too new and too varied for packaged “black box” drivers
- 10 different applications will use 10 different types of LEDs and/or 10 different configurations of LEDs
- 10 different LED driver designs are needed (at least!)



How Many Paths from AC to CC?

- **Direct non-isolated from AC to LED**
 - Some ‘black box’ solutions, but range of V_O and I_F is limited
 - Safety and code/legal issues without isolation
- **Multiple-stage AC to LED with isolation, PFC**
 - Also some ‘brick’ type solutions. Still not very flexible
- **Intermediate DC bus voltage and DC-DC LED drivers**
 - Most flexible but most expensive: DC bus voltage determines topology of LED driver

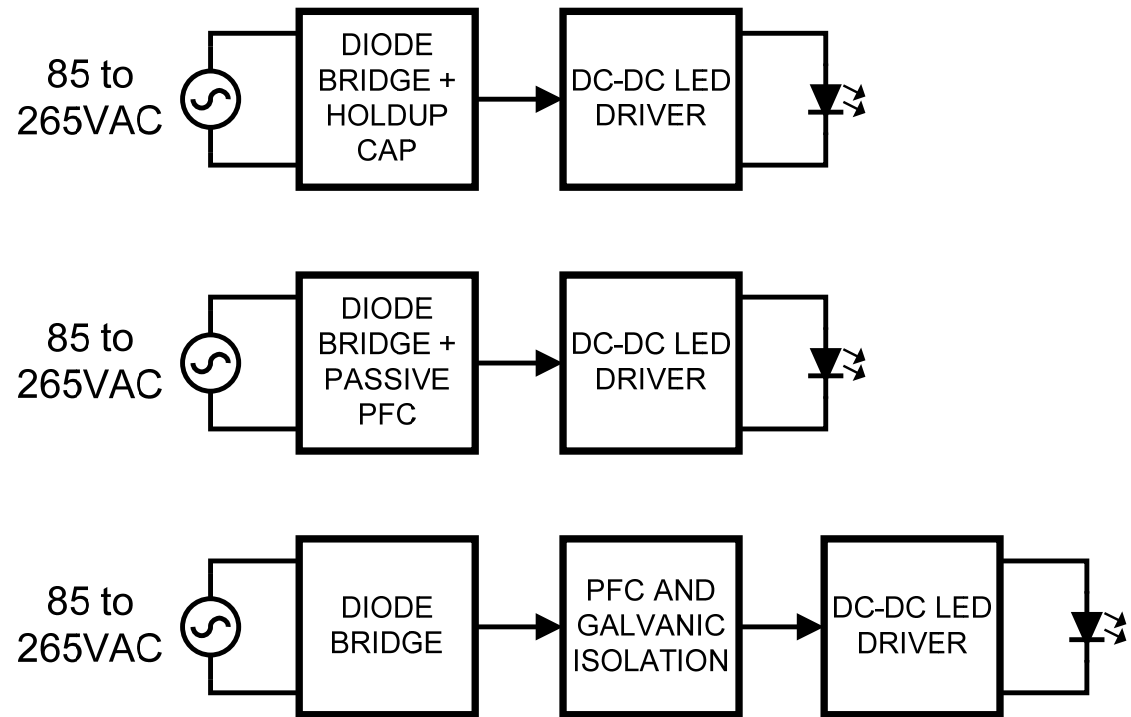

Once the LEDs Have Been Selected

- Lighting designers know how many lumens they want
- They know the color temperature or the wavelength needed
- Ex. City streetlight, uses total 64 LEDs
 - Input is 110VAC: output is up to 200W depending on LED current
 - Needs high efficiency and high power factor
 - Replacement for metal halide or high-pressure sodium




1W (350 mA)

2W (700 mA)


3W (1000 mA)

Arraying your LEDs

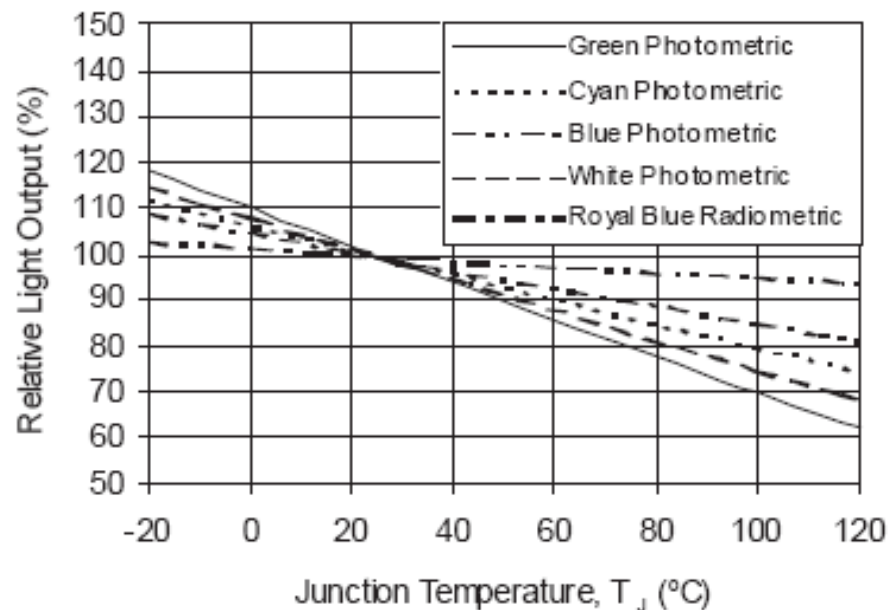- Today's typical 1W LED gives 50 lm/W at 25° C
- Then drops with rising T_j




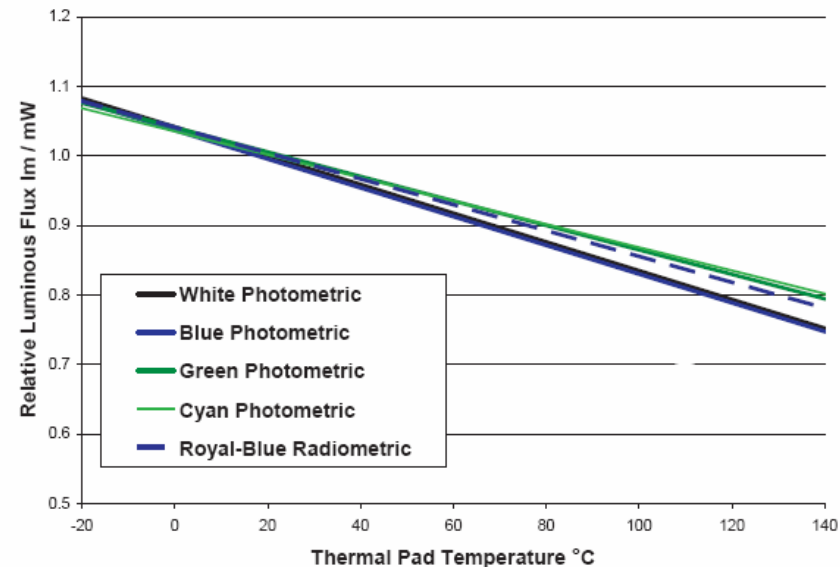- Today's best 1W LED approaches 100 lm/W at 25° C
- Then drops with rising T_j



Most applications need more than one LED!

All In Series

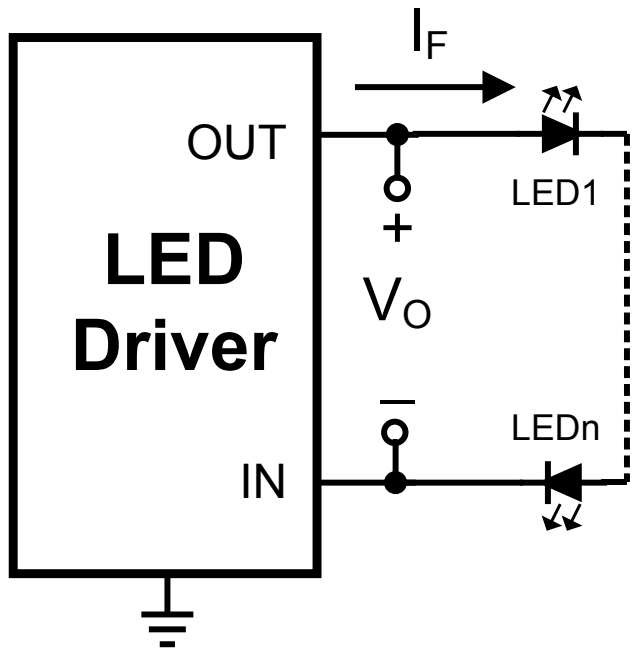


- **Pros:**

- Guaranteed current matching
- Continues to operate if LEDs fail short circuit*

- **Cons:**


- Highest output voltage
 - Component selection thins as voltages go up
 - Safety standards get more strict
- No more light if an LED fails open circuit

Short Circuit LED Failures in Series

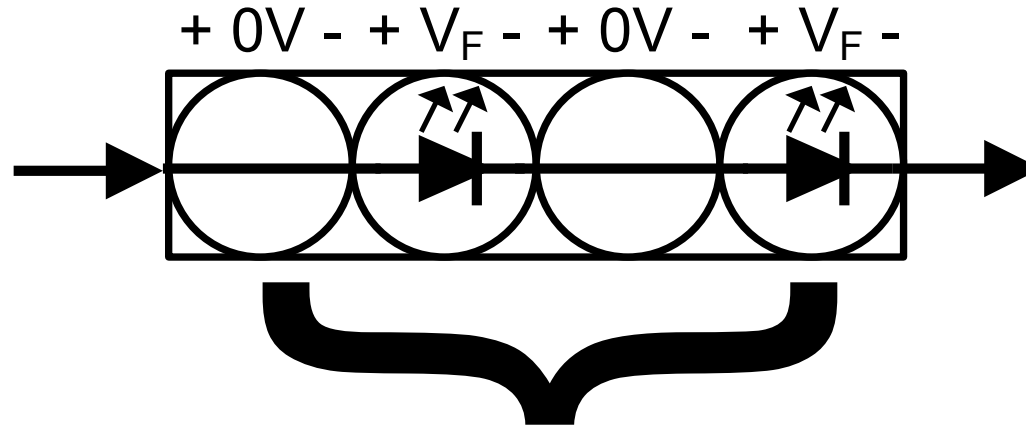


- LED do fail short circuit (not as often)
- Voltage across short is usually near-zero
- Total output voltage decreases
- How many LEDs can fail before the lamp is considered 'dead'?

Open Circuit LED Failures in Series

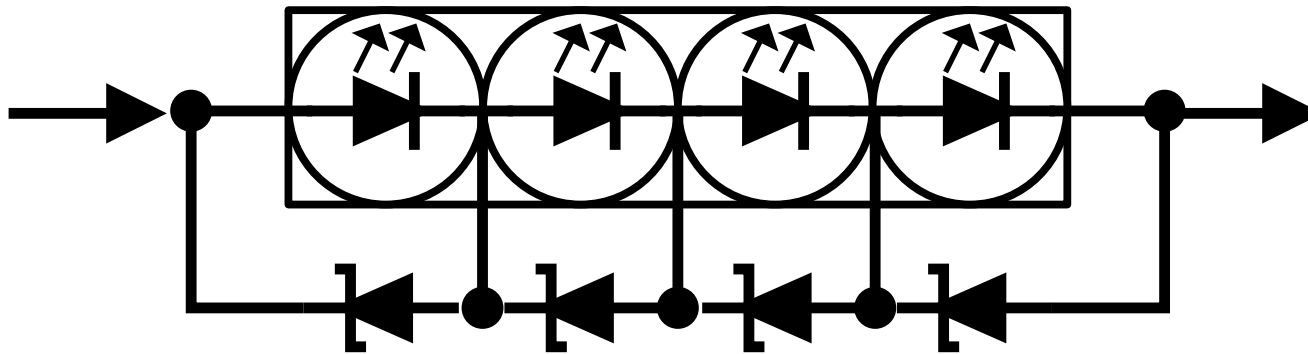

- Anti-parallel zener protection keeps the lamp lit when one LED fails open circuit
- Zener breakdown V_Z must be higher than V_{F-MAX}
- Zener must be fairly high power
- Again, how many LEDs can fail before the lamp is considered 'dead'?

Series-Parallel

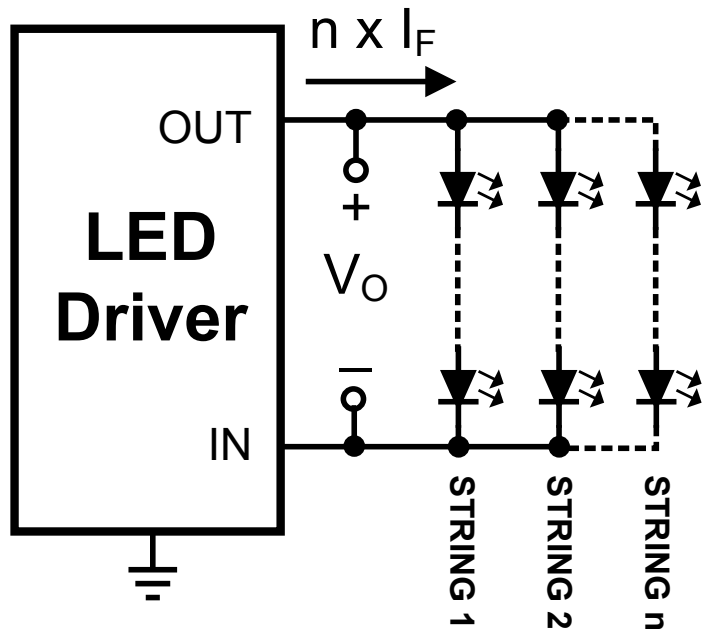

- **Pros:**

- Lower V_O
 - Staying within safety limits
- Continues to operate if LEDs fail short circuit*

- **Cons:**


- **No current matching**

- V_F varies from LEDs, even LEDs from same wafer
- V_F drops with T_J , potential positive feedback loop

Pitfall of Series-Parallel #1

- Ballast resistors work well with a voltage source and a low current LED
- The old way:
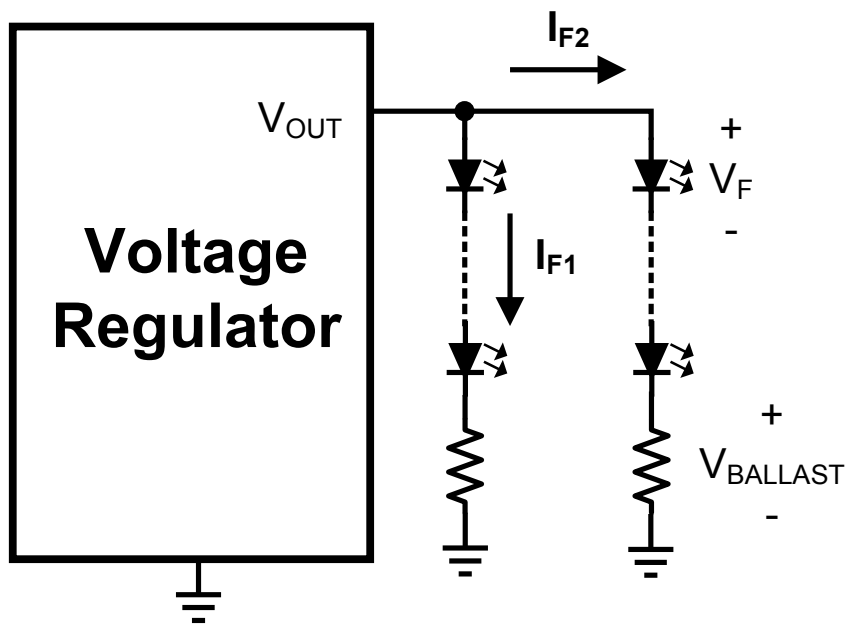
$$I_F = \frac{V_O - n \times V_F}{R_{BALLAST}}$$




The tolerance of I_F improves:


- As I_F decreases
- As $R_{BALLAST}$ increases
- As $V_{BALLAST}$ increases

Pitfall of Series-Parallel #2

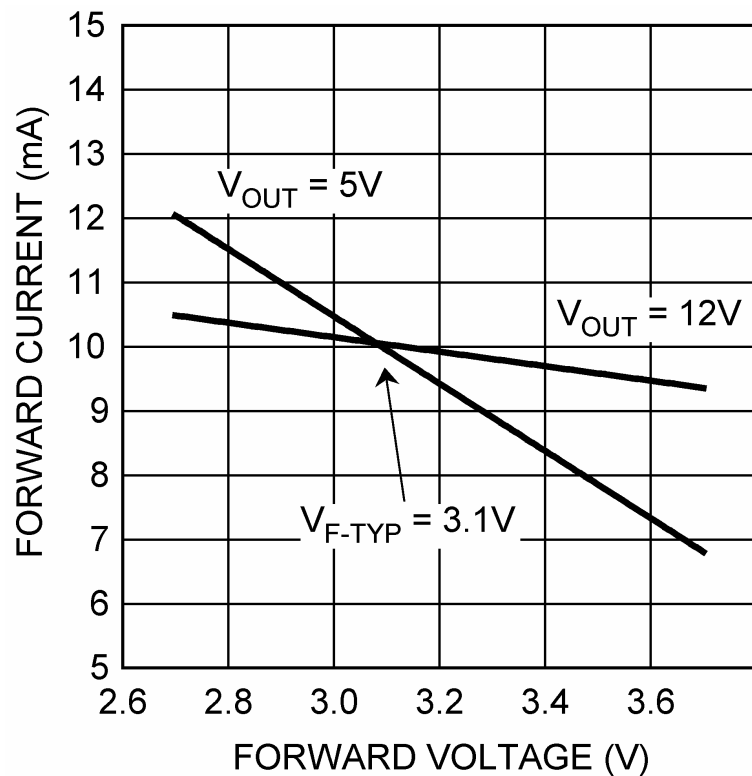- LED current accuracy drops at high current
- Dissipation in R_{BALLAST} goes up quickly





10 mA White LED

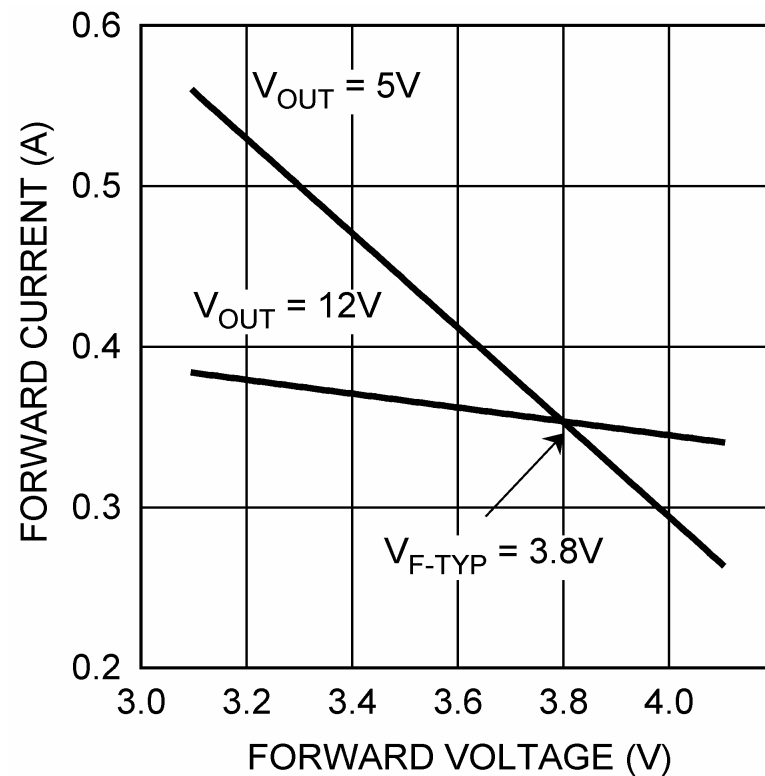

350 mA White LED


Pitfall of Series-Parallel #3

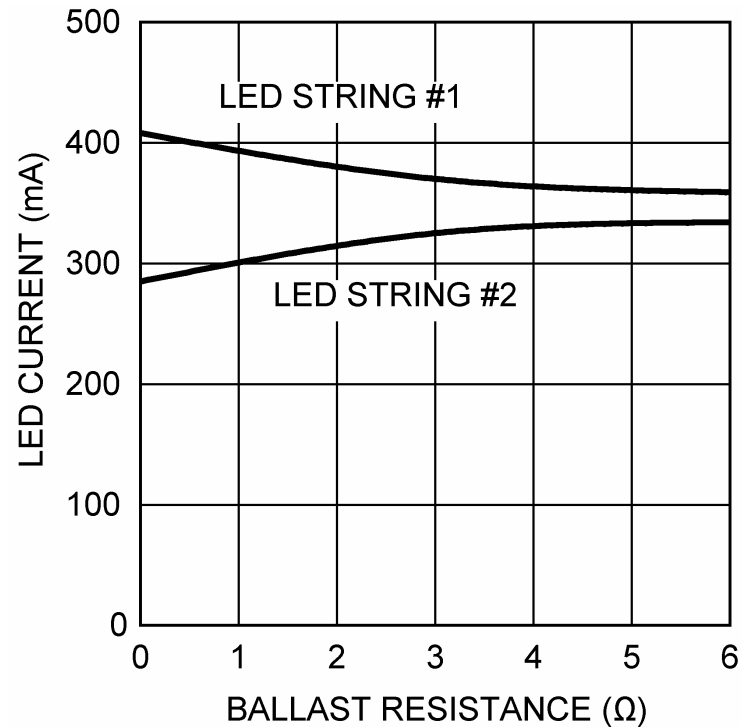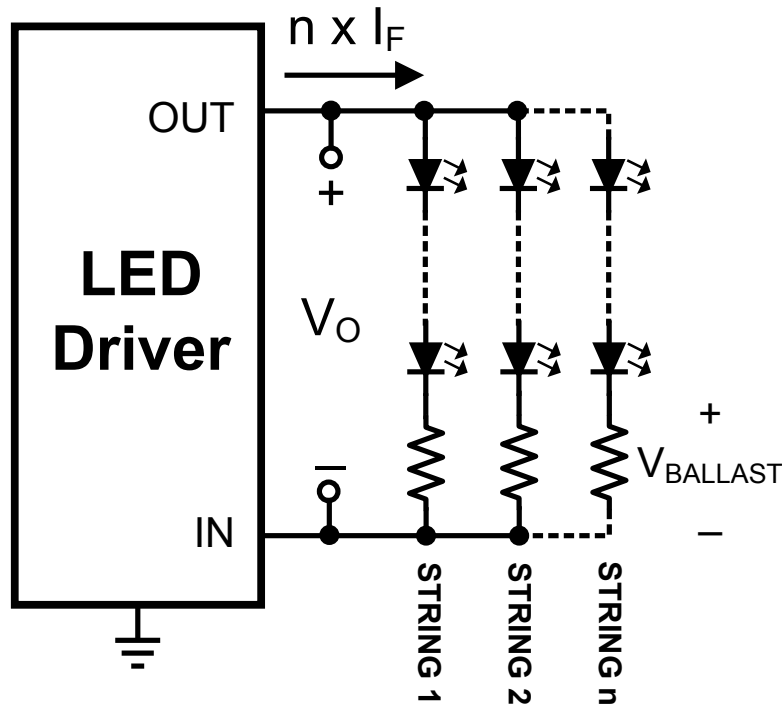- Ballast resistors make a current source no better than a voltage source
- Ratio of dynamic resistance, r_D to R_{BALLAST} determines the improvement in I_F matching




Poor Fault Response with Series-Parallel

- Open Circuit

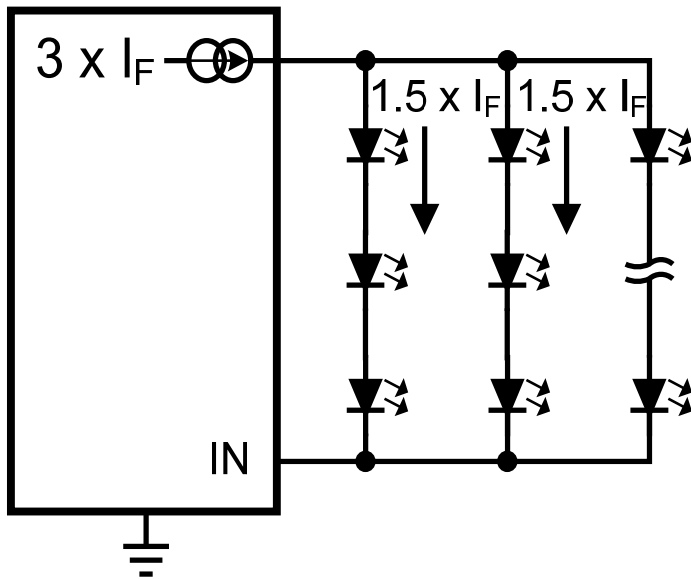


- Short Circuit

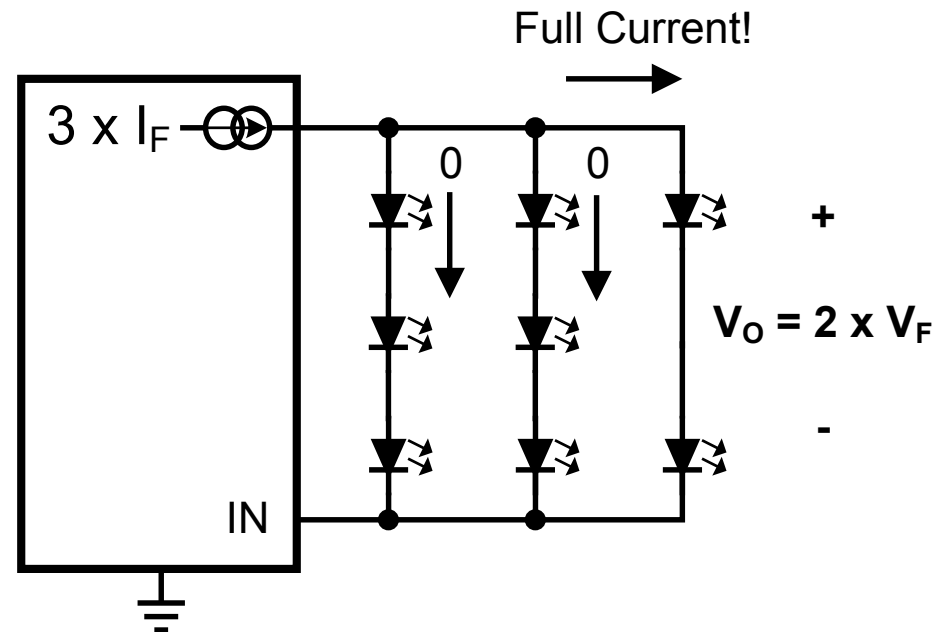

- This assumes that the LED driver is a pure current source

Multiple Regulators


- V_O can stay low for safety

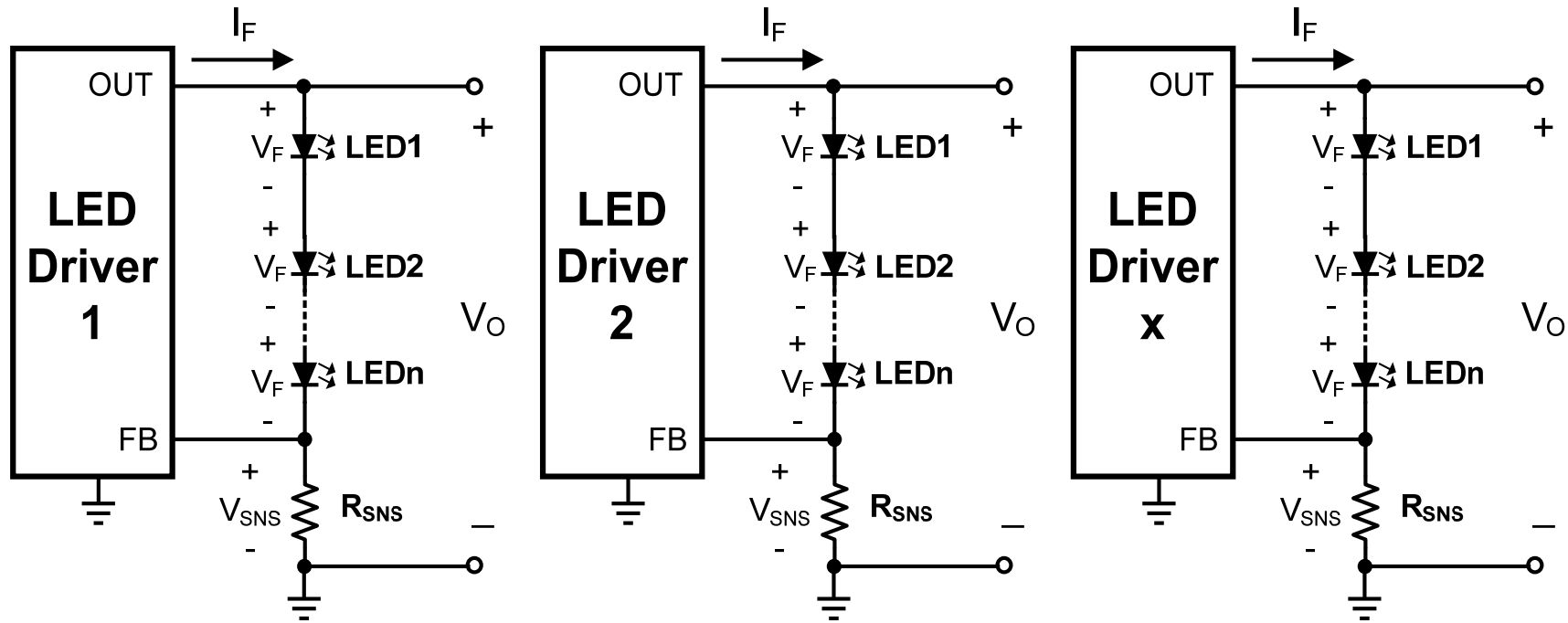


- Best performance when an LED fails:
 - Open circuit: $(1 - x) / x$ LEDs still operating
 - Short circuit: $n * x - 1$ LEDs still operating*

Determine the Total Output Current

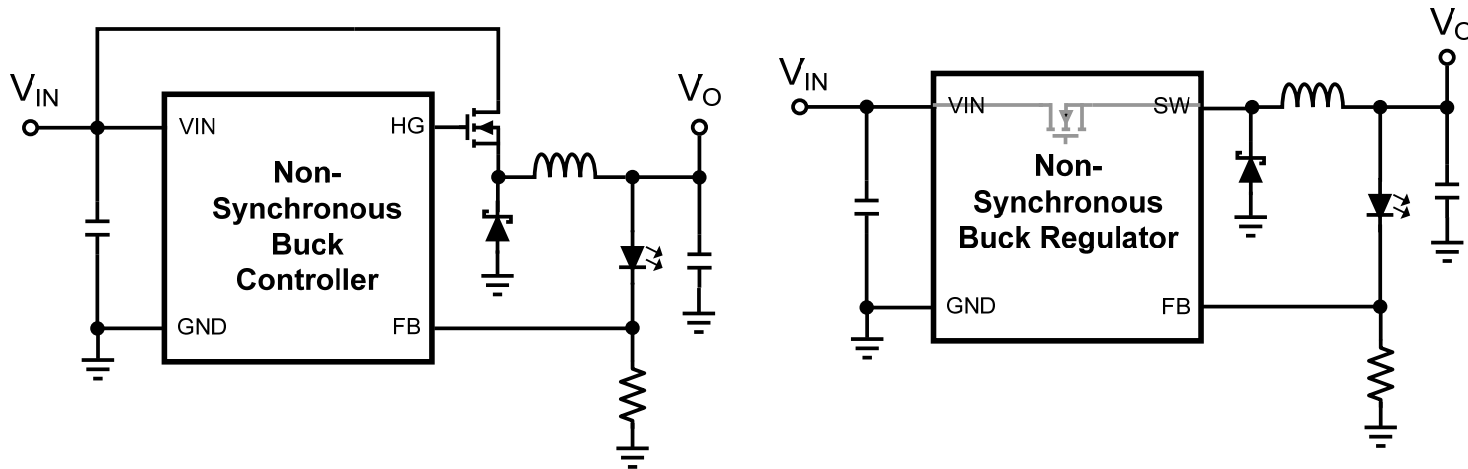- Linear Regulators are generally cost effective up to ~150 mA
- Switching Regulators (internal power switches) are generally cost effective up to 3A
- Switching Controllers (external power switches) are used above 3A



Control I_F , but know full V_O Range

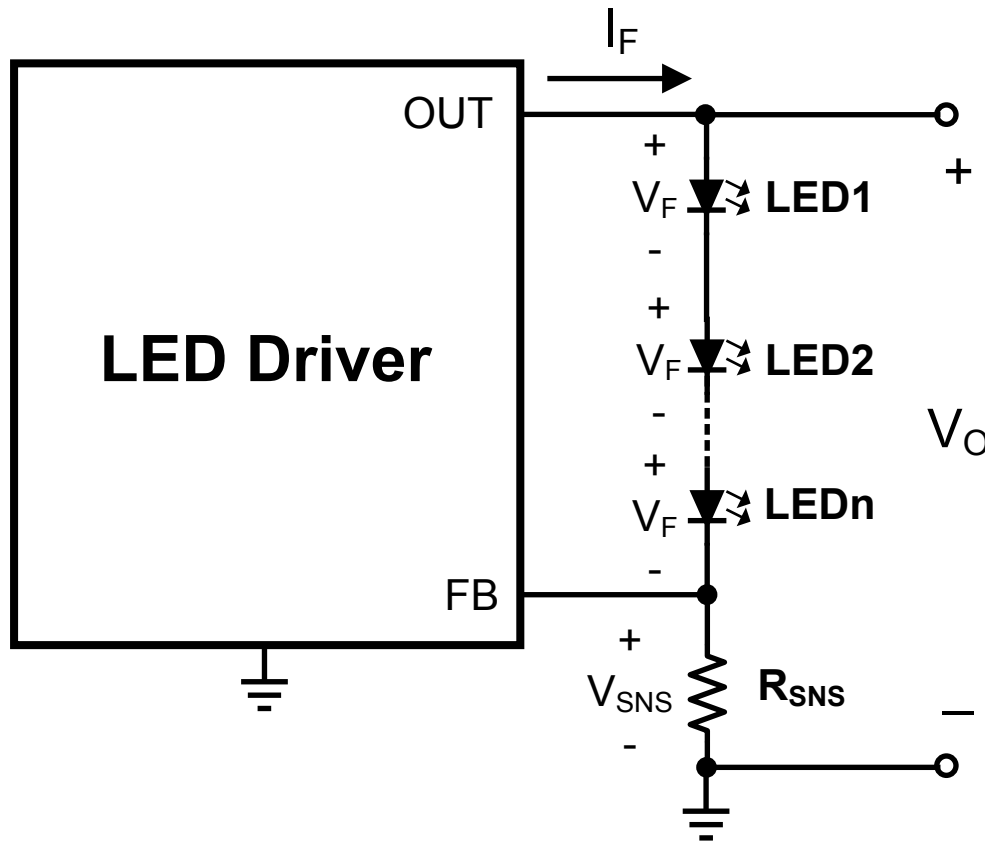

Typical I_F Drive
Currents:

-350 mA

-700 mA

-1000 mA



-1500 mA

-2A, 2.8A and
increasing

$$V_O = n \times V_F + V_{SNS}$$


LED Types by Chemistry and V_F

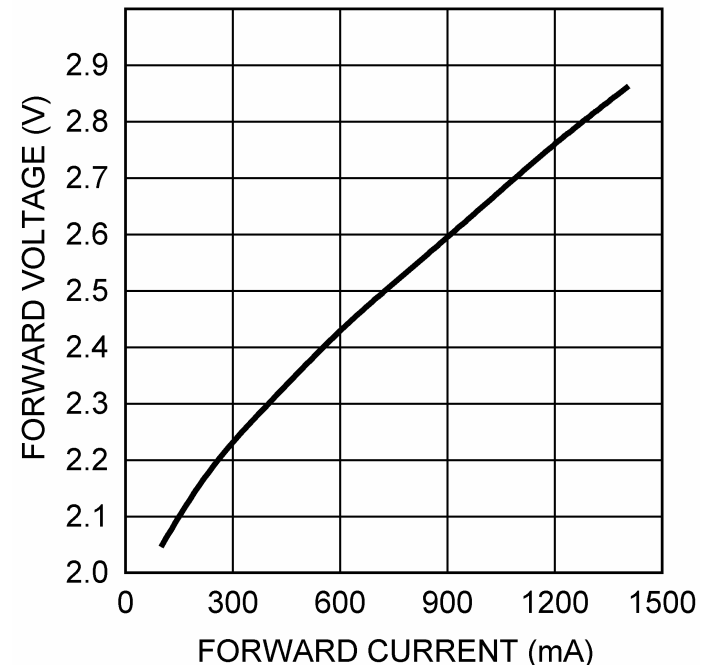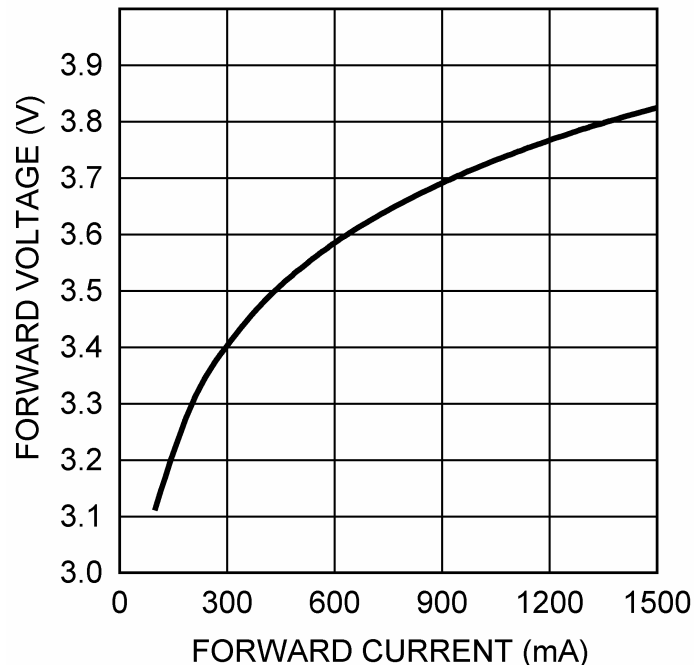- InGaN used in deep green, blue, and WHITE
- Forward voltage, V_F of 3V to 4V (typical)
- AllnGaP used in red, orange, amber
- Typical V_F is 2V to 3V



Dynamic Resistance as a Load

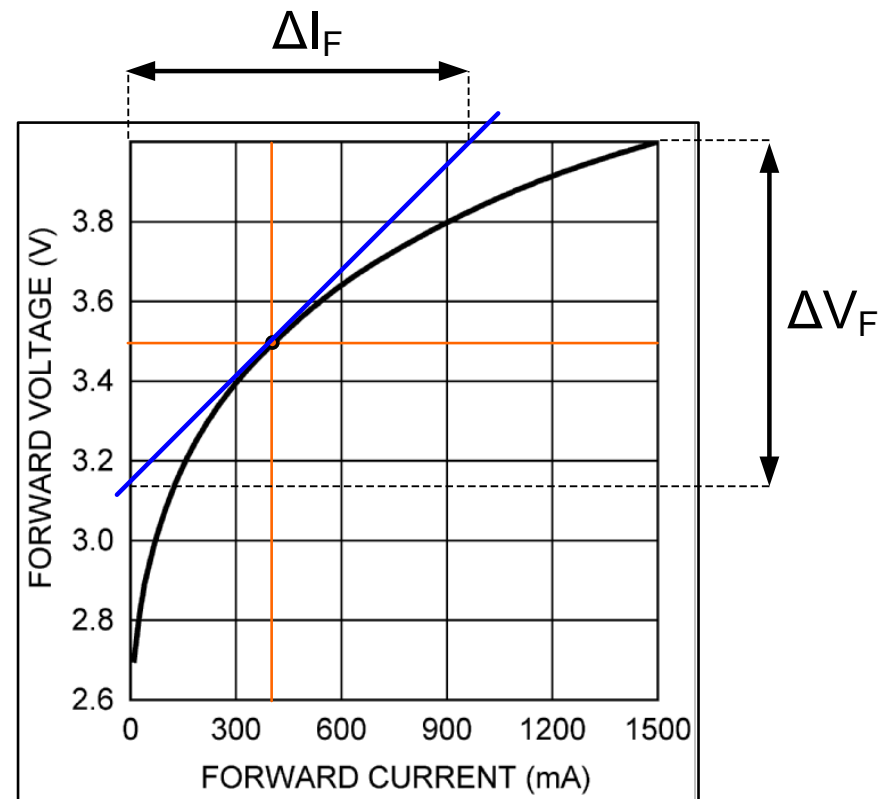
- Dynamic Resistance, r_D , is the inverse of the I_F vs. V_F curve
- r_D is typically 5x to 10x lower than the result of simply dividing V_{F-TYP} by I_{F-TYP}
- The control loop sees r_D , so the load impedance $Z_L = r_D + R_{SNS}$
- Comparator-based regulators like hysteretic and constant on-time still use r_D to select the output filter capacitance



$$r_D = \frac{\Delta V_F}{\Delta I_F}$$

Input Voltage Can be Almost Anything

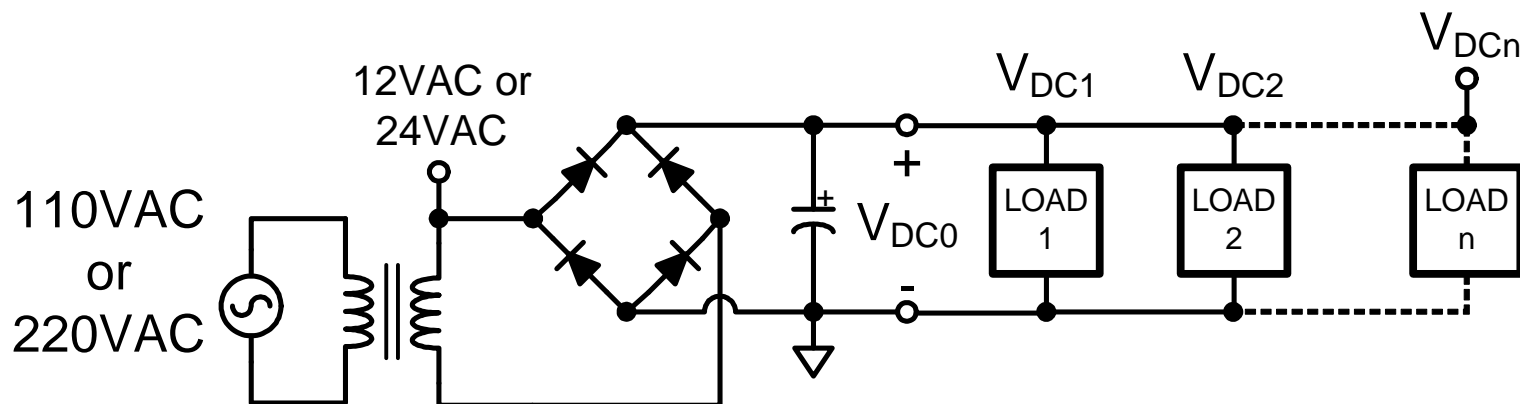- DC Rails have a tolerance
 - Ex. 24V \pm 2%, 5%, 10%....
- Rectified AC has a tolerance




$$V_{DC0} > V_{DC1} > V_{DC2} > V_{DCn}$$

LED Driver Design Outline

1. Determine I_F and V_F range for each LED
2. Fix the arrangement of all LEDs
3. Identify total output current, voltage, power
4. Determine regulator type based on P_{OUT} and relative V_{IN} and V_O
5. Design power supply taking into account LEDs as a load
6. Use a dedicated LED driver IC whenever possible

LED Driving from AC Mains


AC to CC

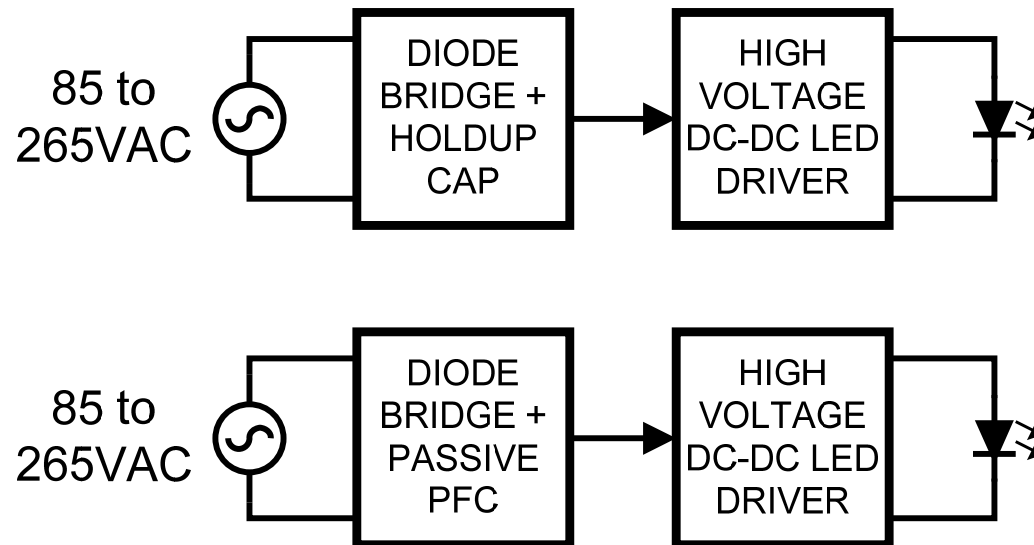

LM3445: Constant Off-Time Controller with Triac DIM Decoder for AC Inputs up to 277VAC

- V_{IN} range: 7V-14V
- Q1: High voltage FET
- Integrated 300 Ω bleeder resistor for proper TRIAC operation
- Simplified Constant Off Time control scheme keeps ripple current constant
- Angle detector/decoder translates TRIAC chopped waveform to analog or digital DIM signal
- Over-current protection with 10 μ s fixed off-time
- DIM is I/O which allows master-slave control in multi-chip solutions.

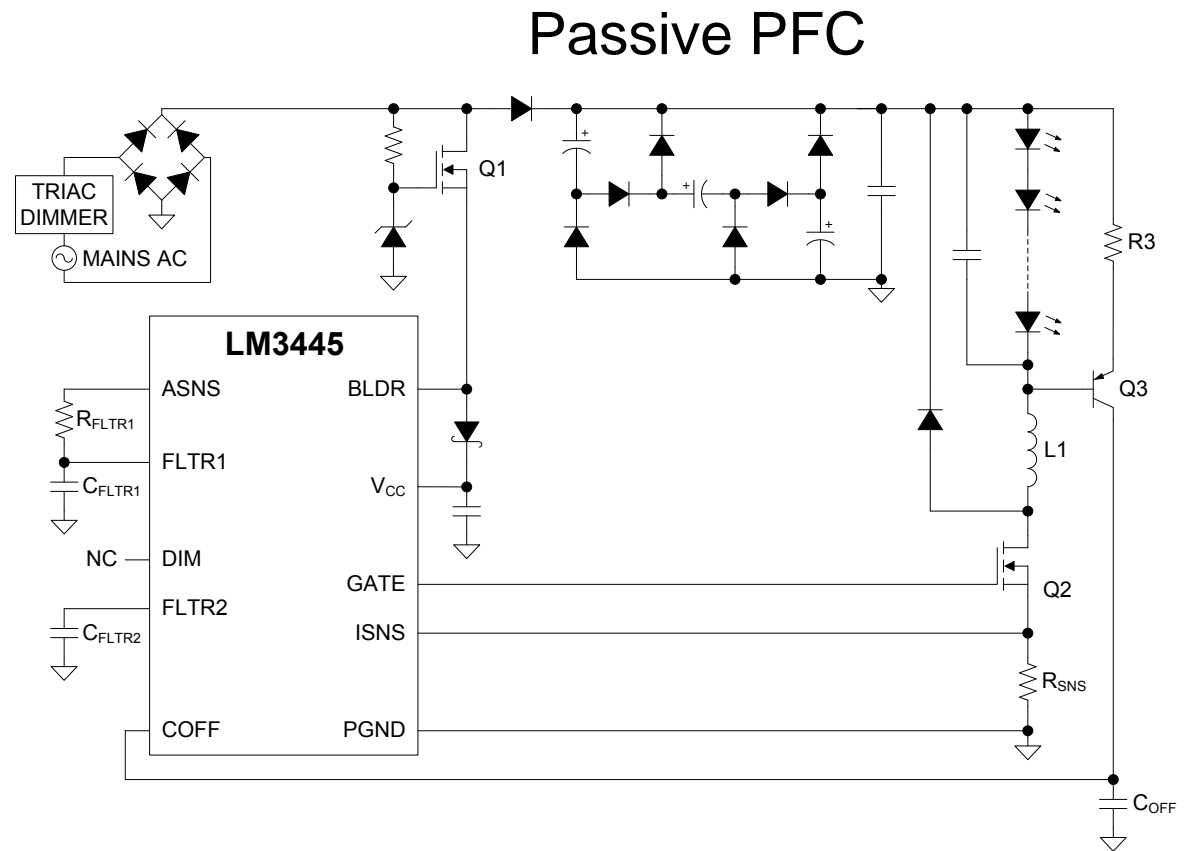Target Applications:
Triac dimmer retro-fit




Triac or PWM Dimming




Triac Characteristics

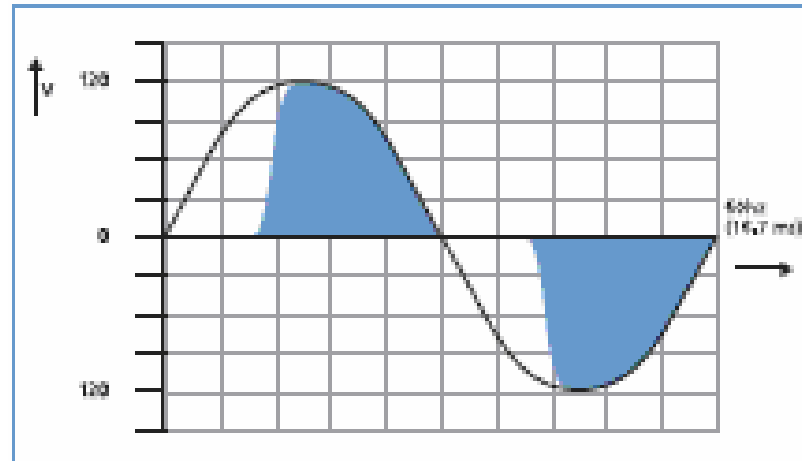- **Triac requires a resistive load to fire**
 - Drip current of 10-15mA
 - Once Triac fires, drip current can be removed to increase efficiency
- **Output is a sampled segment of the offline AC waveform**
 - Based on the firing angle set by the Triac dimmer




Forward phased Triac-dimmed waveform

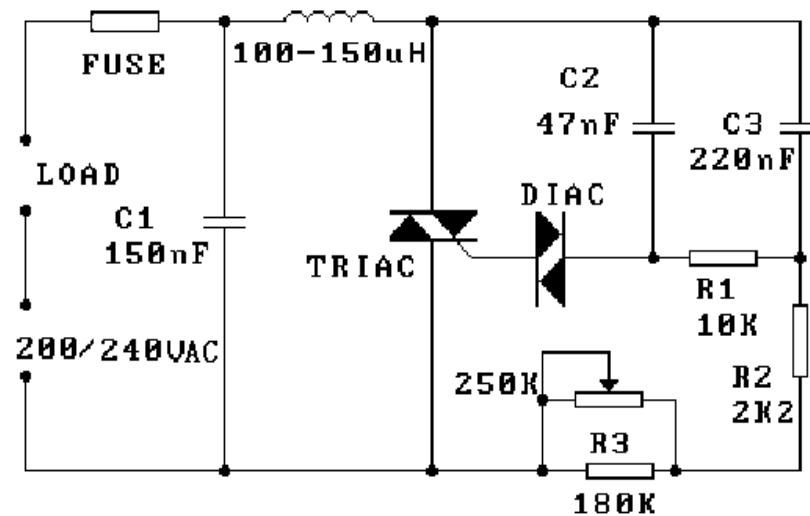


LED Driving from DC Inputs

DC to CC

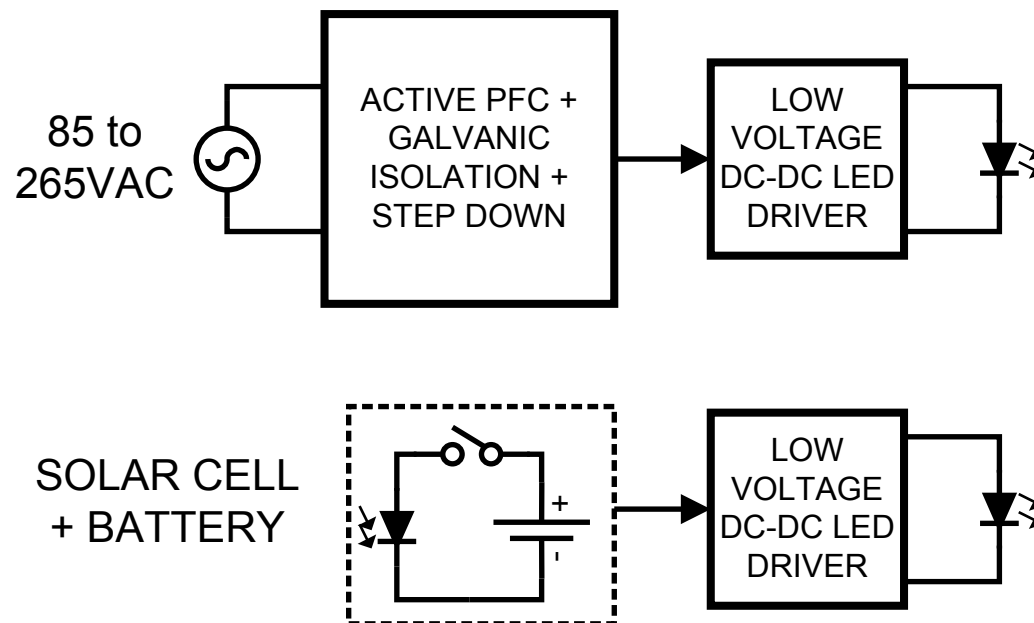

Select Topology of LED Driver: Buck

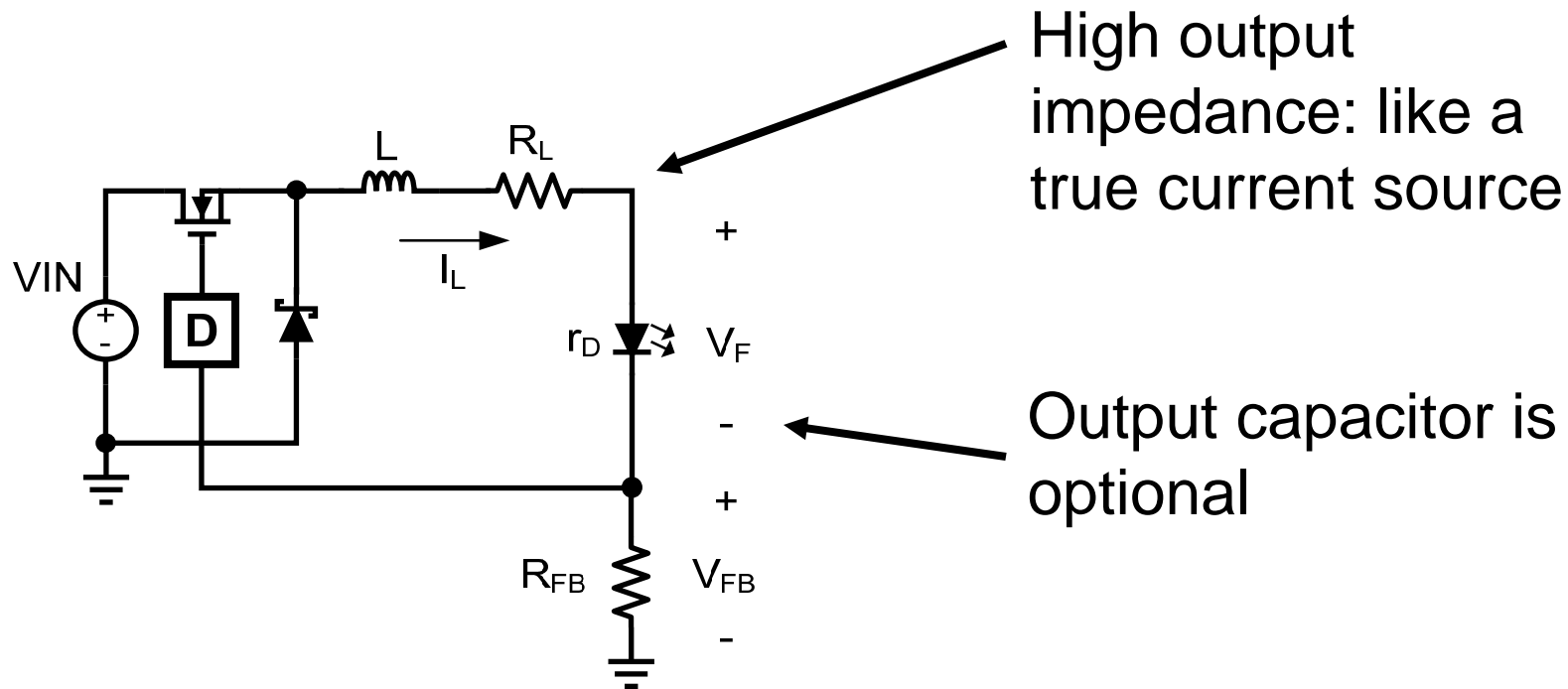- **Buck is best – use whenever possible**



- **I_F slew rate is limited only by L , V_{IN} , V_F**

LM3401: PFET Controller, Buck Current Source for High Power LEDs

External Power FET

- Controls output currents up to 4A

100% Duty Cycle Capable

- Best for circuits that run close to dropout


Tiny MSOP-8 Package

- Similar size, comparable thermal performance to PSOP-8

Adjustable Safety Current Limit

Hysteretic Control with Adjustable Window

- User sets LED ripple current

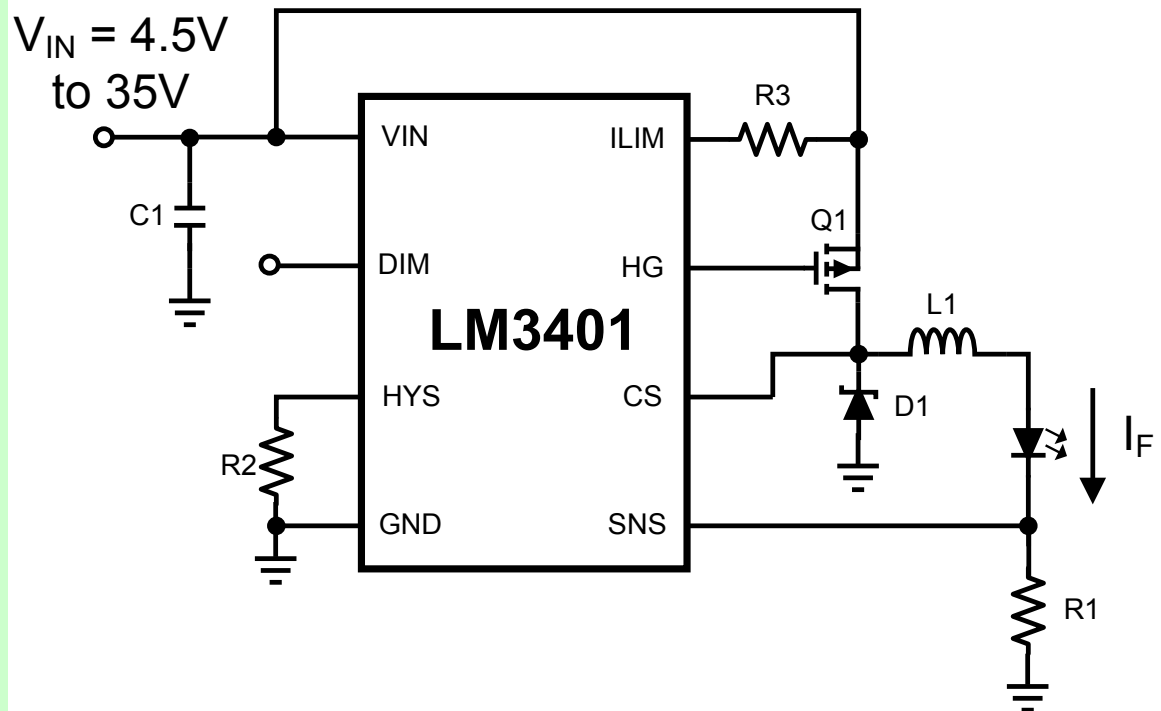


LM3406/06HV: 1.5A Buck Current Source Driver for High Power LEDs

Has All Features of LM3402 and LM3404 Plus:

- **Dedicated Error Amplifier**
 - Provides True Average LED Current Control
- **Senses V_O and Adjusts on-time**
 - Keeps f_{SW} constant over V_{IN} AND V_O
- **eTSSOP-14 Package**
 - Similar size, comparable thermal performance to PSOP-8
- **Adds Input Comparator for “Two-Wire Dimming”**
 - Eliminates one wire from harness

V_{IN} still 6V to 42V (LM3406)


V_{IN} still 6V to 75V (LM3406HV)

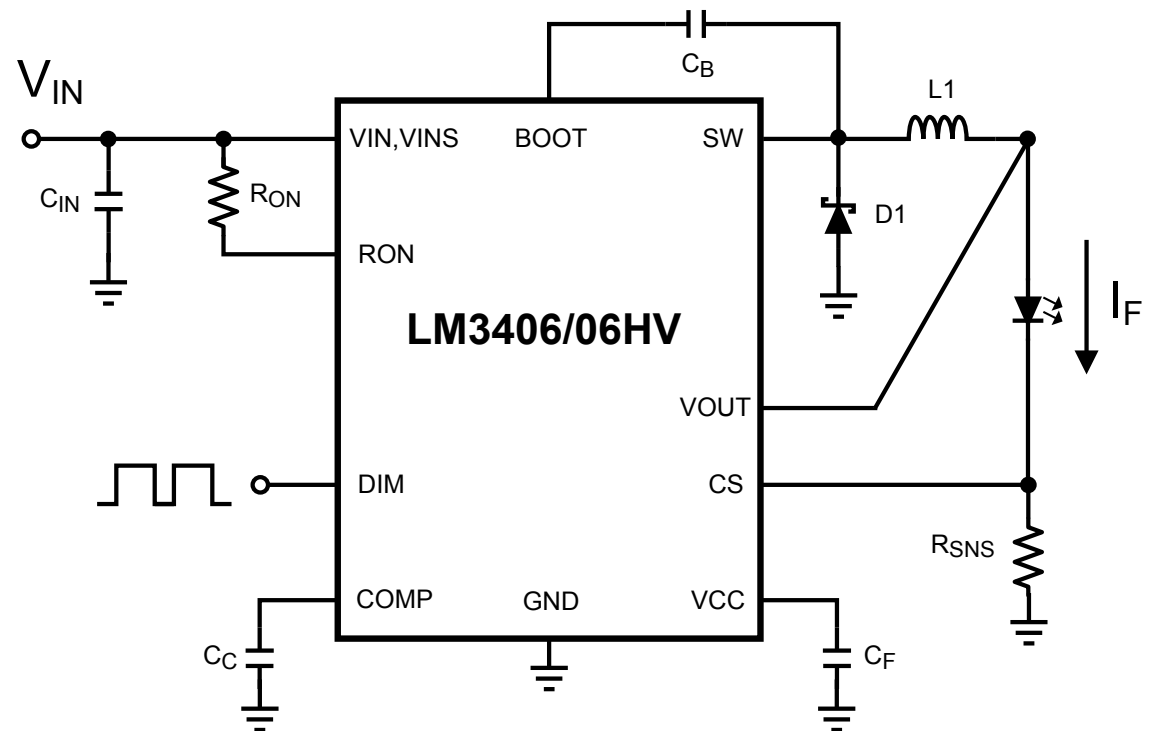

LM3409/09HV: High-Side PFET Buck Controller for LEDs

Key Features:

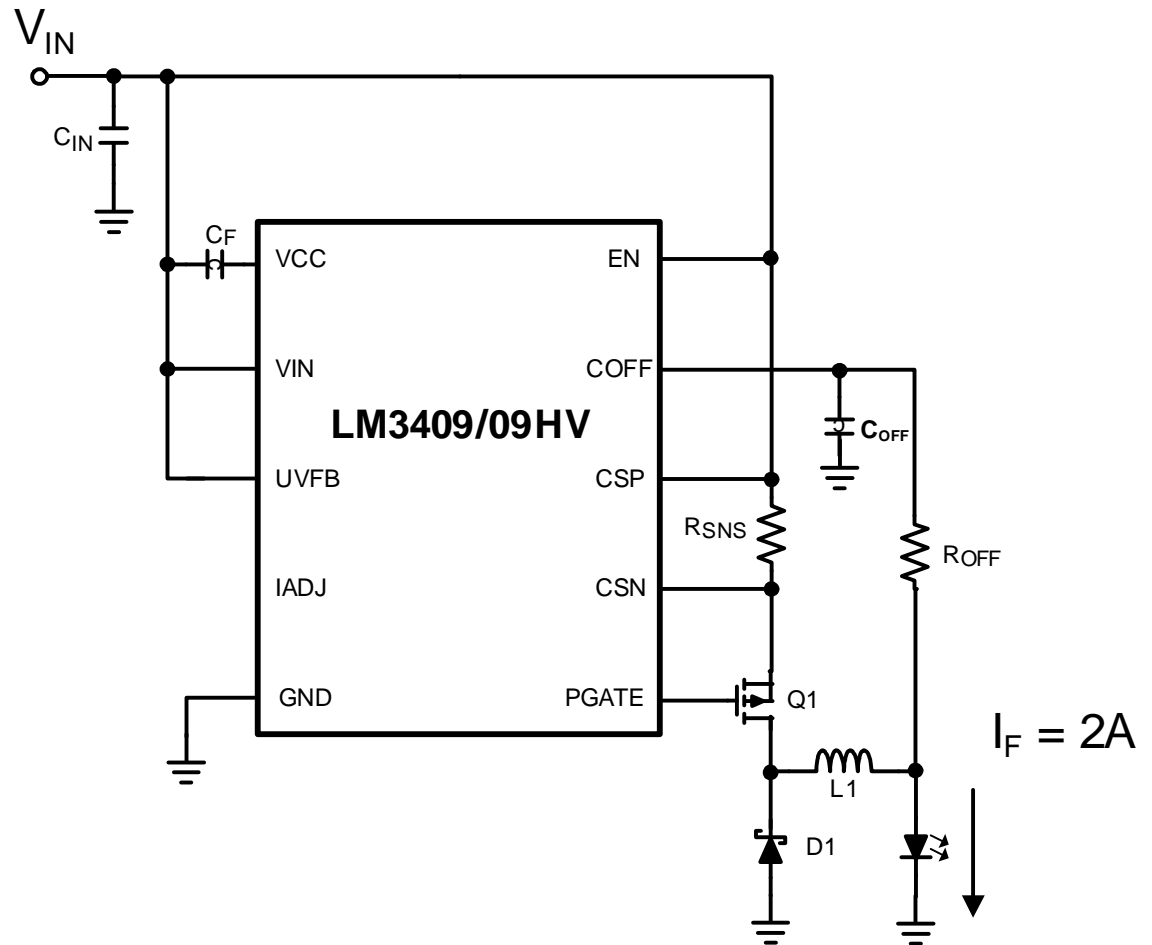- V_{IN} 6V to 42V (LM3409)
- V_{IN} 6V to 75V (LM3409HV)
- External power PFET
 - 100% Duty Cycle Capable
 - Output Currents up to 4A
- Differential, high-side current sense
 - Simplifies system wiring
- PWM dimming and analog dimming at 1000:1
 - Similar size, comparable thermal performance to PSOP-8
- No control-loop compensation




Select Topology of LED Driver: Boost

- Necessary when $V_o > V_{in}$

Continuous input current -> low EMC

Output capacitor is mandatory

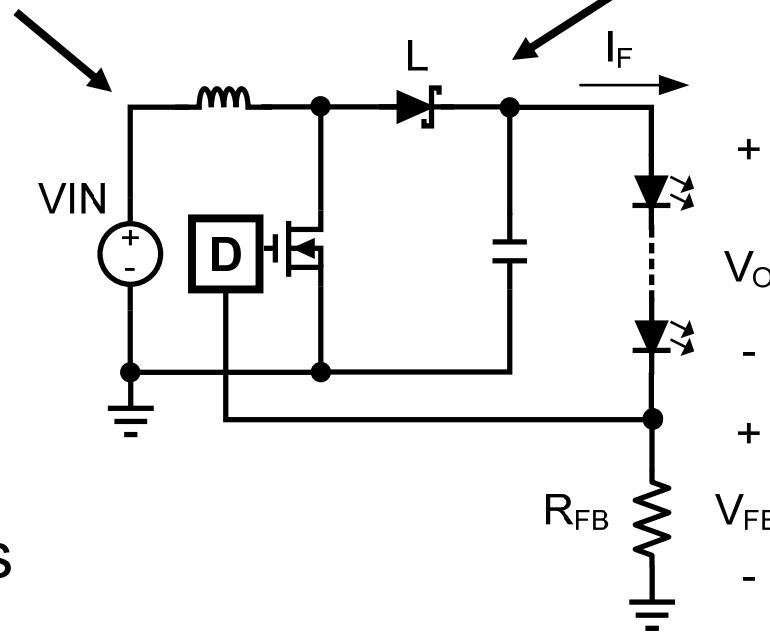

Power efficiency almost as good as buck


Must have output open-circuit protection

LM3421/23/29: Low Side Controllers for Constant Current LED Drivers

Key Features


- V_{IN} Range: 4.5V to 75V
 - To Accommodate Cold Crank and Load Dump Conditions
- Fast (50 kHz) PWM dimming input, Programmable frequency
 - For greater design flexibility
- Dimming MOSFET gate driver
 - High-side dimming
- Zero current shutdown, LED ready flag, fault timer pin, Input UVLO, High side current sensing
 - For greater system reliability
- Drives 1W, 3W, and higher powered LEDs

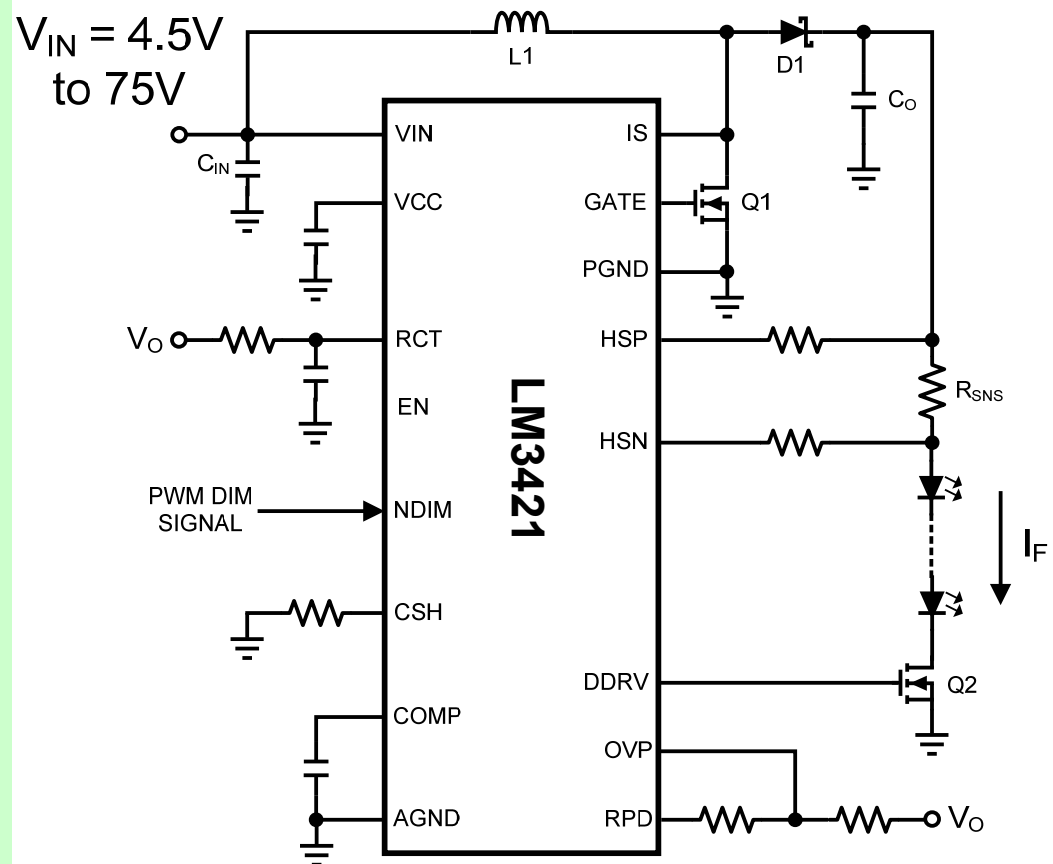Boost, Buck, Buck-Boost, SEPIC Topologies




LM342x Family Options


LM3423

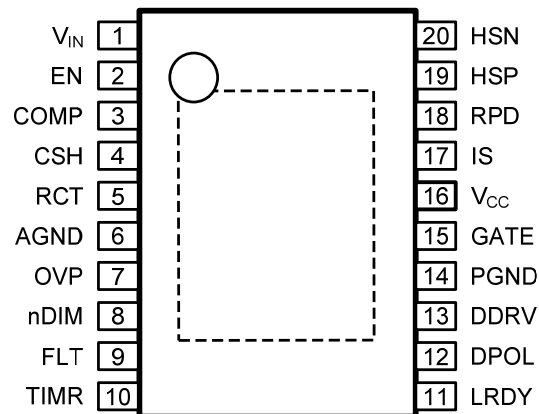

LM3421

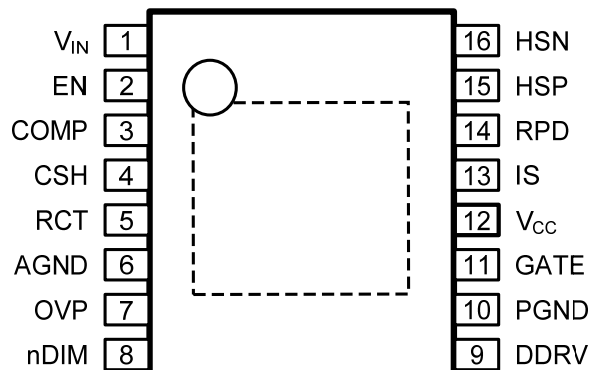


LM3429

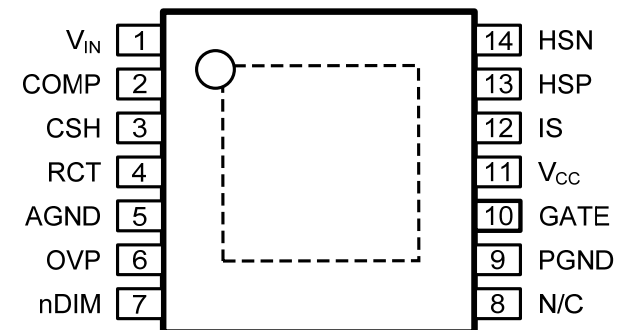


Buck-boost: Last Resort

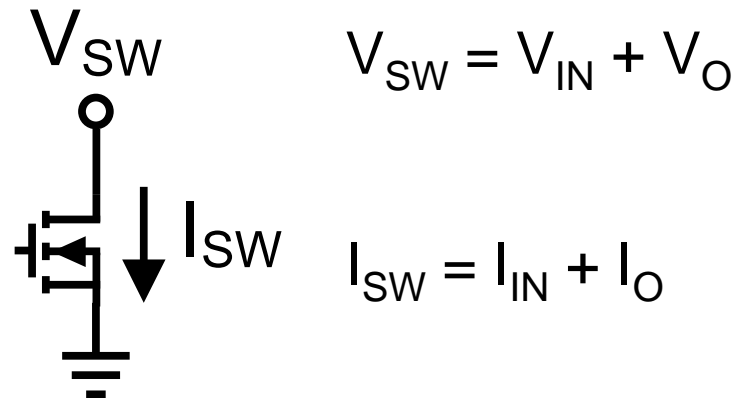- May invert the polarity of V_O (single inductor buck-boost, Cuk)
- May regulate V_O with respect to V_{IN}
- May require two inductors (SEPIC, Cuk)
- May require a transformer (Flyback)
- May require up to four switches
- Are always less efficient than buck or boost
- High voltage and current stress in power switch



LM3421/23 SEPIC with Fast Dimming

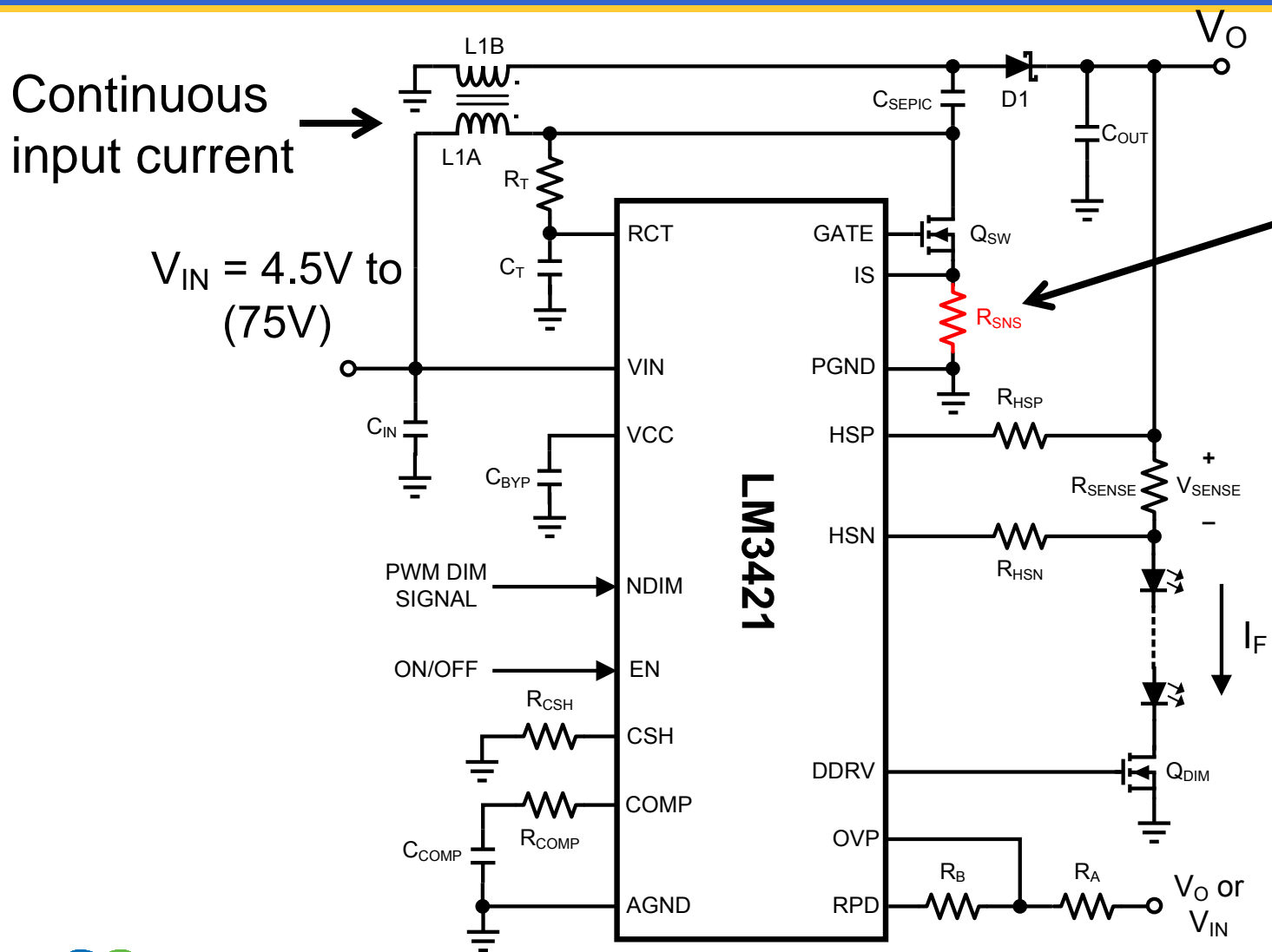


National's Online Tools Allows Easy Design and Analysis

LED WEBENCH® Online

1. Choose a Part




Enter Specifications

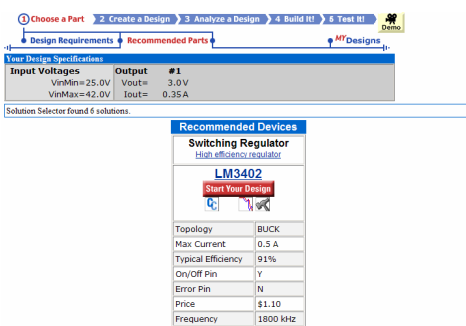


Select Part

2. Create a Design

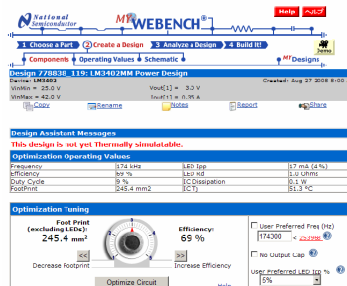

Optimize for Footprint and Efficiency

3. Analyze a Design

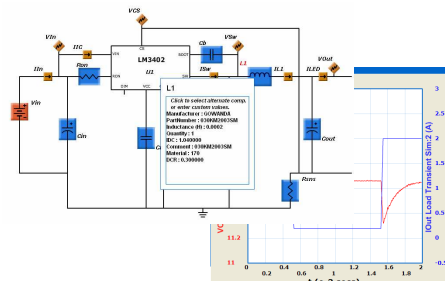

Generate Schematic/
Electrical Analysis

4. Build It!



Order Evaluation Board







National Offers a Large Portfolio of Lighting Reference Designs!

LED REFERENCE DESIGN LIBRARY

Reference Design Selection Tool

46 designs found.

46 ready designs

NSC Part Used	View Reference Design in WEBENCH®	Get Report	Description	PADC ID	Vin min (V)	Vin max (V)	Vout max (V)	Iout (A)	Pout (W)	Efficiency (%)	Switch Freq (kHz)
LM2623	Open Design		LM2623 Boost regulator LED driver;	PADC_NSC0119	1.5	3.3	3.5	0.35	1.22	84.0	2000
LM2623A	Open Design		High efficiency, step-up regulator LED driver for battery-powered and low input voltage systems;	PADC_NSC0498	1.8	3.4	3.5	0.65	2.28		2000
LM2698	Open Design		LM2698 8x4 LED array driver with PWM dimming;	PADC_LED005	5.0	5.0	16.0	0.16	2.56		1250
LM2700	Open Design		LM2700 Boost converter LED Driver; constant current source;	PADC_NSC0247	2.7	3.6	3.0	1.0	3.0		1250
LM2700	Open Design		LM2700 Boost Luxeon V LED driver with PWM dimming;	PADC_NSC0336	2.4	4.5	5.4	0.7	3.78		1250
LM2737	Open Design		Solar cell input LED driver that drives one high power LED at 2A; PWM dimming;	PADC_LED002	12.0	14.0	3.0	2.0	6.0		2000

URL: <http://www.national.com/webench/ledrefdesigns.do>

PowerWise® Initiative

- **PowerWise Devices**
 - Products selected by strict power-to-performance efficiency metrics in 25 product categories
- **PowerWise Subsystems**
 - Complementary devices act as a unit provide optimal mix of low power consumption and heat
- **PowerWise Architectures**
 - Novel implementations of technology (digital and analog) that dramatically lowers system-level energy consumption

