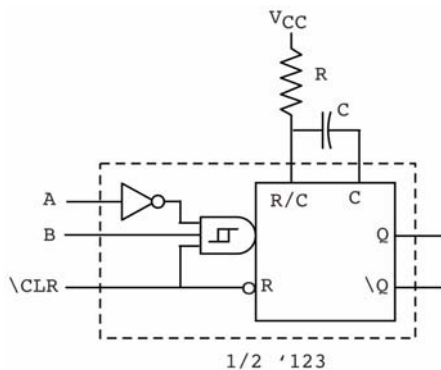


TIMING CIRCUITS

- one-shots
- timer 555
- counting with FF
- 555 oscillator
- relaxation oscillator
- VCO


MONOSTABLE MULTIVIBRATOR (ONE-SHOTS)

- Generates a fixed length output pulse after receiving a trigger signal. The pulse length is determined by external RC network



1/2 '123

\overline{CLR}	A	B	Q	\overline{Q}
0	X	X	0	1
1	0	1	1	0
1	1	0	0	1
1	0	1	1	0

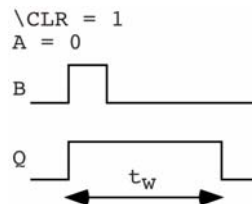

$$t_w [ns] = 0.28 R_x [k\Omega] C_x [pF] \left(1 + \frac{0.7}{R_x [k\Omega]} \right) \quad \text{for } C_x > 1000pF$$

- 74123
- 4538: CMOS
- 74121: 74221 dual '121
- 74423


One-shot Parameters

- input gating
- retriggerability
- resettability
- pulse width

TIMER 555


General purpose variable timing device:

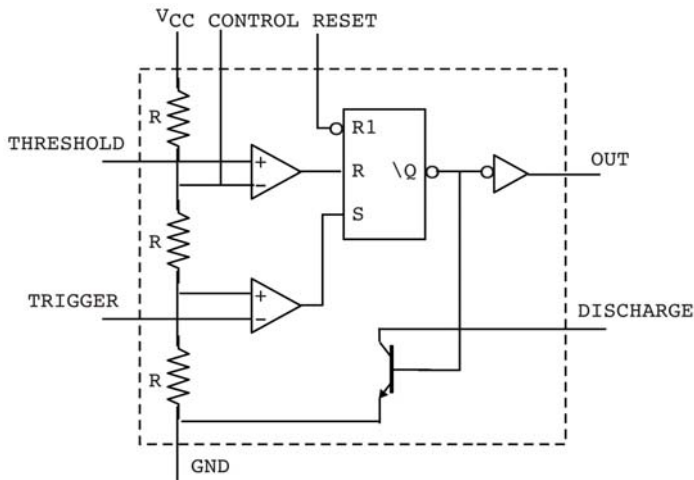- monostable multivibrator (pulse generator)
- astable multivibrator (oscillator)
- ramp generator
- pulse width modulation
- pulse position modulation




Function Table

reset	trigger	threshold	OUT	discharge
L	X	X	L	on
H	$< \frac{1}{3} V_{CC}$	X	H	off
H	$> \frac{1}{3} V_{CC}$	$> \frac{2}{3} V_{CC}$	L	on
H	$> \frac{1}{3} V_{CC}$	$< \frac{2}{3} V_{CC}$	n.c.	n.c.


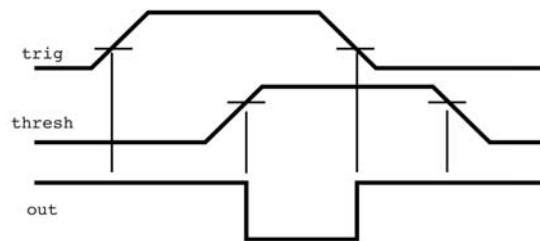


COUNTING WITH FF

Divide-by-2



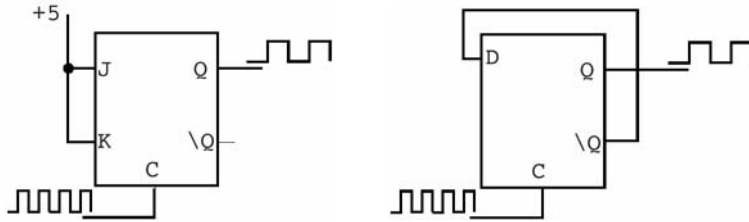


Divide-by-2^N: Binary Ripple Counter

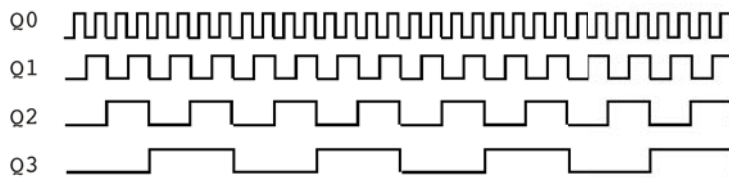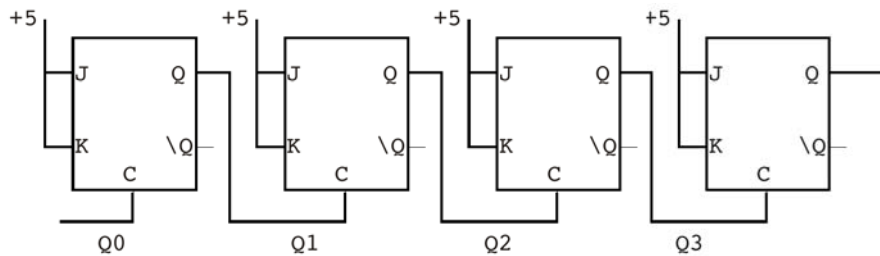

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
...
1	1	1	0
1	1	1	1
0	0	0	0
0	0	0	1

Dived-by-Three Synchronous Counter

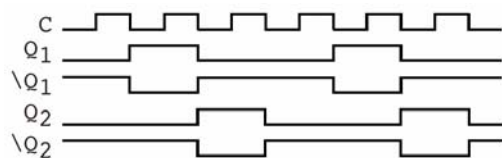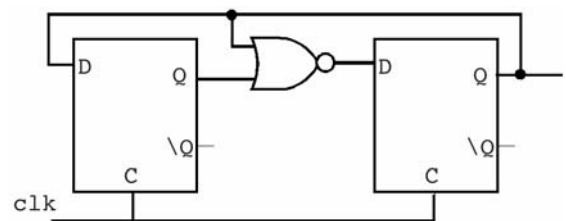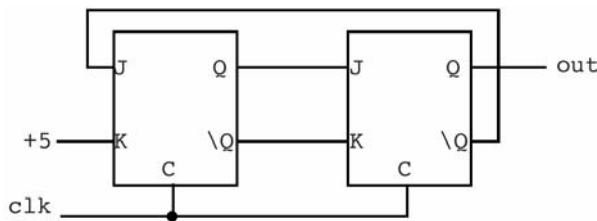

Pulse Train Synchronizer

- using SR FF and D register

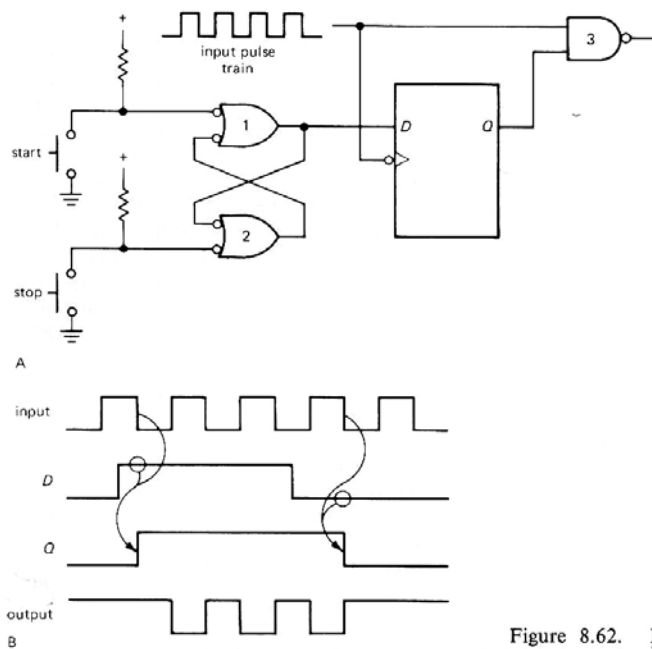


Figure 8.62. Pulse-train synchronizer.

Counters

- binary counter: 74393
- BCD counter: modulo-10 counter: 74390
- modulo-n counter
- cascading
- ripple counter
- synchronous counter
 - 74160-163: 4-bit synchronous
 - 74590,592: 8-bit synchronous
- up/down counter: 74191, 74193, 74569, 74579
- load & clear
- counter + latch: latched data can be displayed while counting continues
- three-state output: 74779
- 74C925-928: counter + latch + 7-seg decoder, driver
- TIL306/7: counter with display
- Intersil 7216: 8-bit 10MHz universal counter, w. display

OSCILLATORS


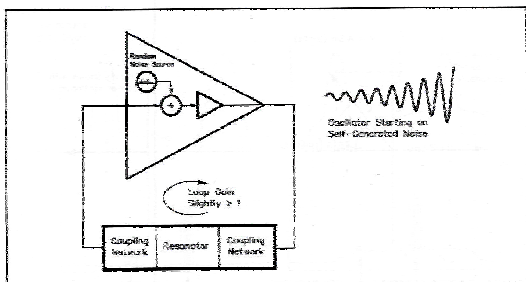
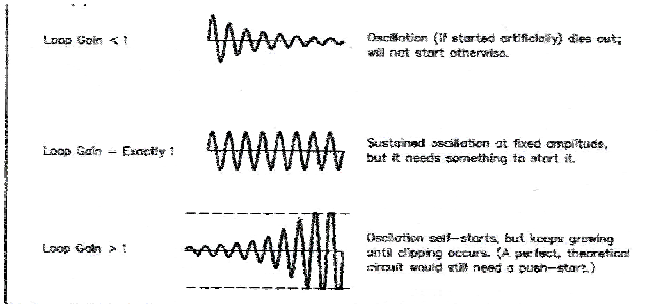
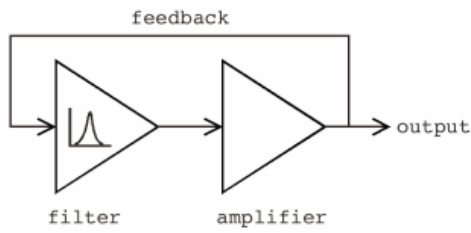


Fig 14.5 — An oscillator with noise. Real-world amplifiers, no matter how quiet, generate some internal noise; this allows real-world oscillators to self-start.

OSCILLATOR WITH 555

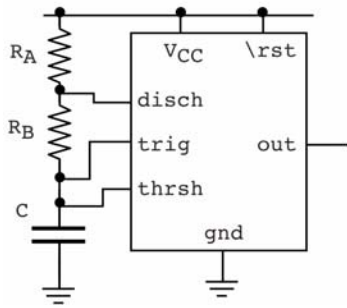


$$Q = 0 \quad V_{trig} = 0 \quad \therefore \text{trigger} \Rightarrow \text{OUT} = \text{Hi}$$

$$V_r = V_{th} = 0 \rightarrow \frac{2}{3} V_{CC} \Rightarrow \text{OUT} = \text{Lo}$$

Disch = on


$$V_r = V_{th} = \frac{2}{3} V_{CC} \rightarrow \frac{1}{3} V_{CC} \Rightarrow \text{OUT} = \text{Hi}$$

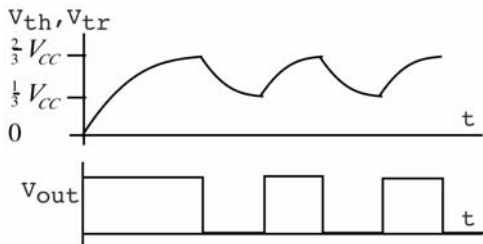Charge through $R_A + R_B$; discharge through R_B



- $T = 0.693(R_A + 2R_B)C$
- duty cycle: $\frac{R_A + R_B}{R_A + 2R_B} \geq 50\%$


Sawtooth Generator

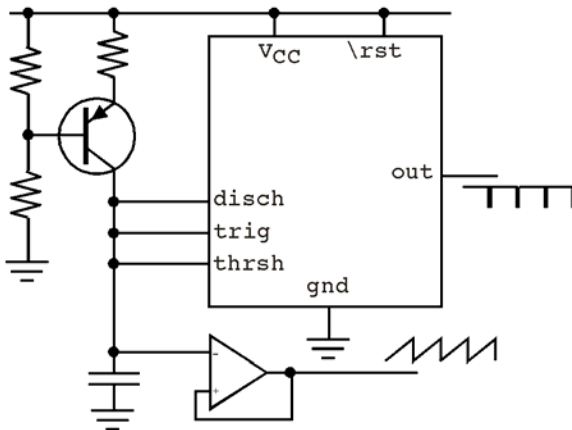

RELAXATION OSCILLATOR

OpAmp circuit with saturation

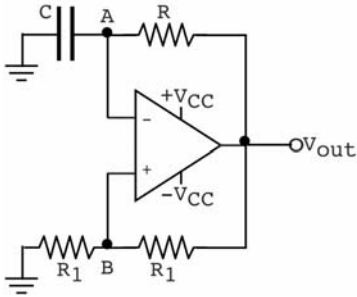Saturation: $\text{If } V_+ > V_- \Rightarrow V_{out} = +V_{CC}$
 $\text{If } V_+ < V_- \Rightarrow V_{out} = -V_{CC}$



$$V_B = \frac{1}{2} V_{out} \text{ always.}$$

If $V_{out} = +V_{CC}$ initially:

Capacitor charges toward $+V_{CC}$

$$V_B = \frac{1}{2} V_{CC}$$

When V_A reaches $V_{CC}/2 \Rightarrow V_- > V_+ \Rightarrow V_{out} = -V_{CC}$

Capacitor discharges toward $-V_{CC}$


$$V_B = -\frac{1}{2} V_{CC}$$

When V_A reaches $-V_{CC}/2 \Rightarrow V_- < V_+ \Rightarrow V_{out} = +V_{CC}$


Repeat from beginning ↴

- $f = \frac{0.45}{RC}$

CMOS Relaxation Oscillator

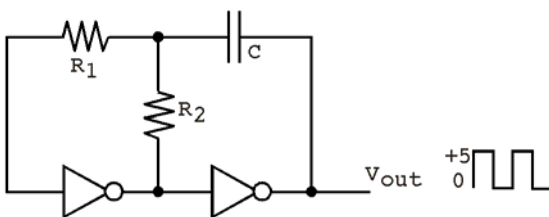

- $R_1 \ll R_2; \quad f \approx \frac{1}{RC}$
- very low noise

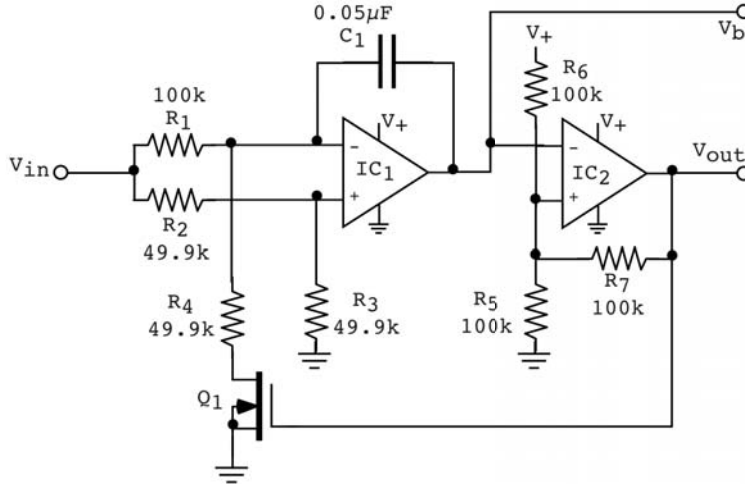VOLTAGE-CONTROLLED OSCILLATOR: VCO**IC₁: Integrator**

If Q₁ is not conducting ($V_{out} = 0$)

$$V_a = V_{in} \frac{R_2}{R_2 + R_3} = 0.5V_{in}$$

$$I_1 = \frac{V_{in} - V_a}{R_1} = \frac{0.5V_{in}}{100k} = (5\mu A/V)V_{in}$$


$$V_b = V_a - \frac{I_1 t}{C_1} = 0.5V_{in} - \frac{5\mu A/V}{0.05\mu F} V_{in} t = 0.5V_{in} - (100)V_{in} t$$

If Q₁ is conducting ($V_{out} = V_+$)

$$I_1'' = \frac{V_a}{R_4} = \frac{0.5V_{in}}{49.9k} = 2I_1$$

$$I_1' = I_1'' - I_1 = I_1$$

$$V_b = V_a + \frac{I_1' t}{C_1} = 0.5V_{in} + (100)V_{in} t$$

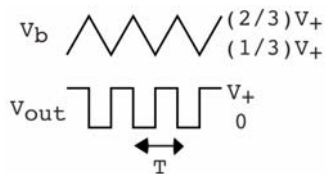IC₂: Schmitt Trigger

$$T = \frac{2}{3} \frac{V_+}{100V_{in}}; \quad f = 150 \frac{V_{in}}{V_+} [Hz]$$

$$0 \leq V_{in} \leq 2(V_+ - 1.5V)$$

- VCO's can also be made from 555 timers.

Function Generator


- VCO + wave shaping
- integrate square wave > triangular wave
- integrate triangular wave > low pass filter > good approx. of sine wave

VCO ICs


- 8038, 2206
- 74LS624-9: 20MHz
- 1648: 200MHz
- VFC, voltage-to-frequency converters: LM331, AD650
- PLL: VCO+phase detector: 4046, 74HC4046

FREQUENCY MEASUREMENTS


Digital Frequency Counter

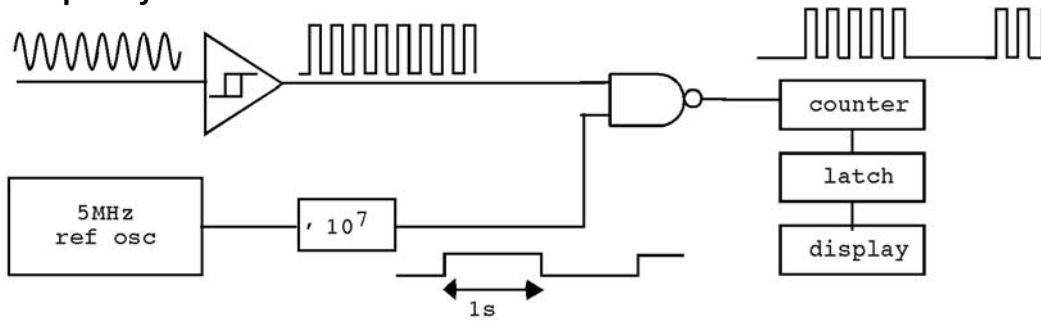


Period (Reciprocal) Counting

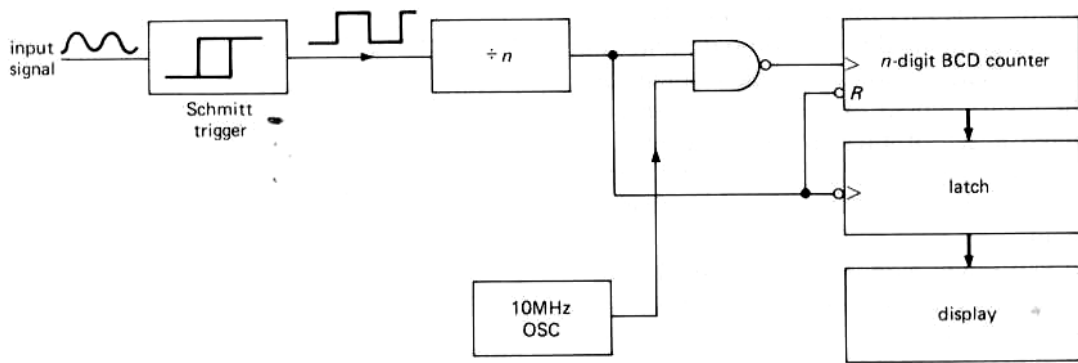

TDC: Time-to-Digital Converter

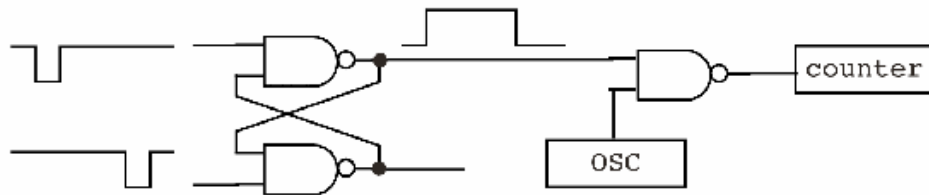

PLL: PHASE-LOCKED LOOP

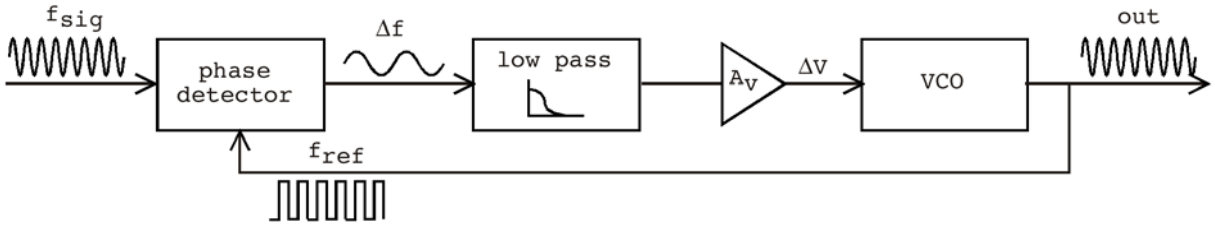

Type I Digital Phase Detector

